


Tutorial 2: Cadence Schematic

Objective:


To introduce the Cadence Virtuoso Schematic and Cadence Analog Design Environment

Procedure:

 1. You will draw the schematic for NAND gate in Virtuoso Schematic



 
2. Test/Simulate your NAND schematic in ADLE
3. Draw a symbol for your NAND circuit



4. Test/Simulate your NAND symbol


First perform the tutorial one again. I have summarize the last tutorial here

Open the cadence software → Enter your UMKC password → It will open a terminal and then enter the following commands

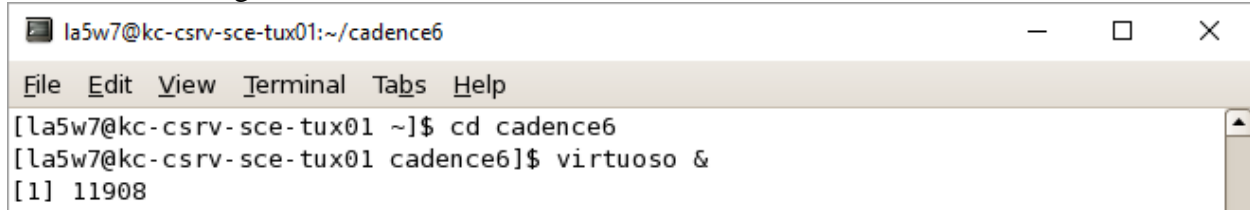A terminal window titled 'la5w7@kc-csrv-sce-tux01:~/cadence6'. The window has a menu bar with 'File', 'Edit', 'View', 'Terminal', 'Tabs', and 'Help'. The terminal content shows the user navigating to the 'cadence6' directory and running the 'virtuoso &' command, which returns the PID '11908'.


```
la5w7@kc-csrv-sce-tux01:~/cadence6
File Edit View Terminal Tabs Help
[la5w7@kc-csrv-sce-tux01 ~]$ cd cadence6
[la5w7@kc-csrv-sce-tux01 cadence6]$ virtuoso &
[1] 11908
```

Creating a Library:

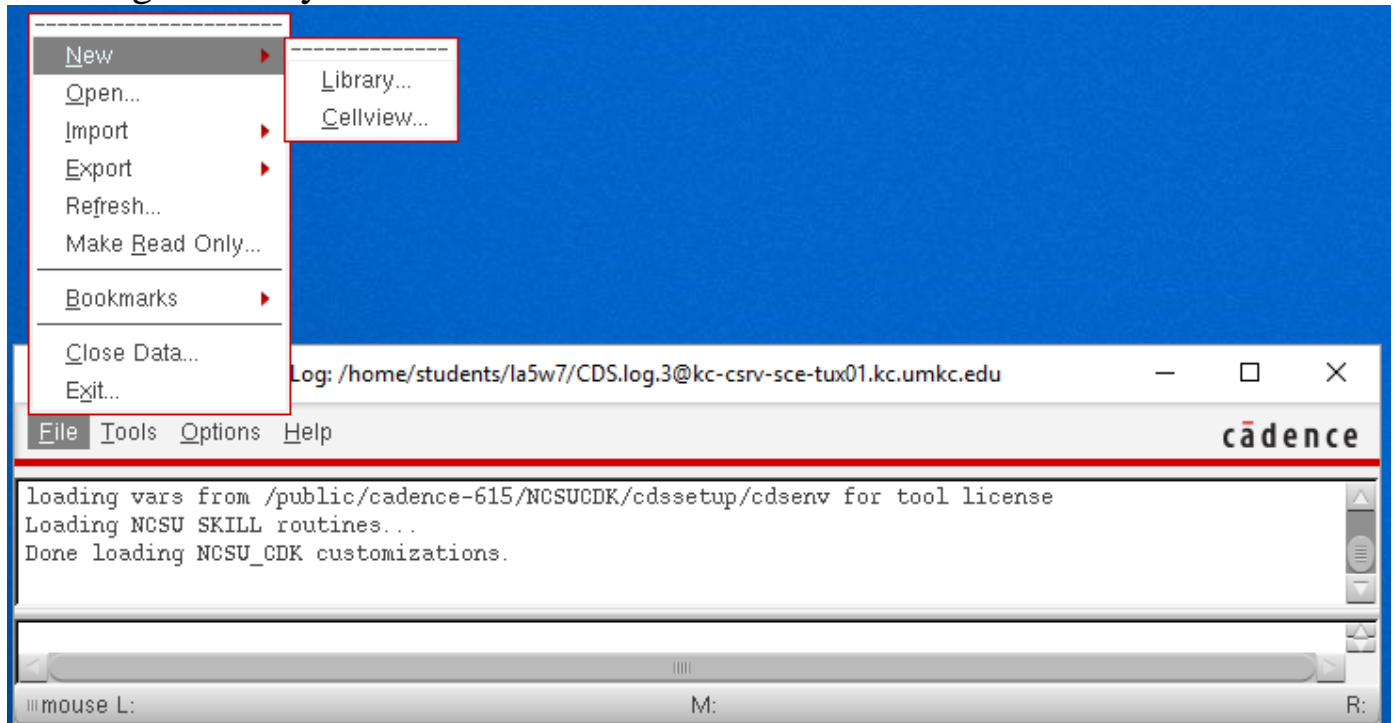


On the New Library window, put a name, click on Attach to an existing technology library button, and then click ok.

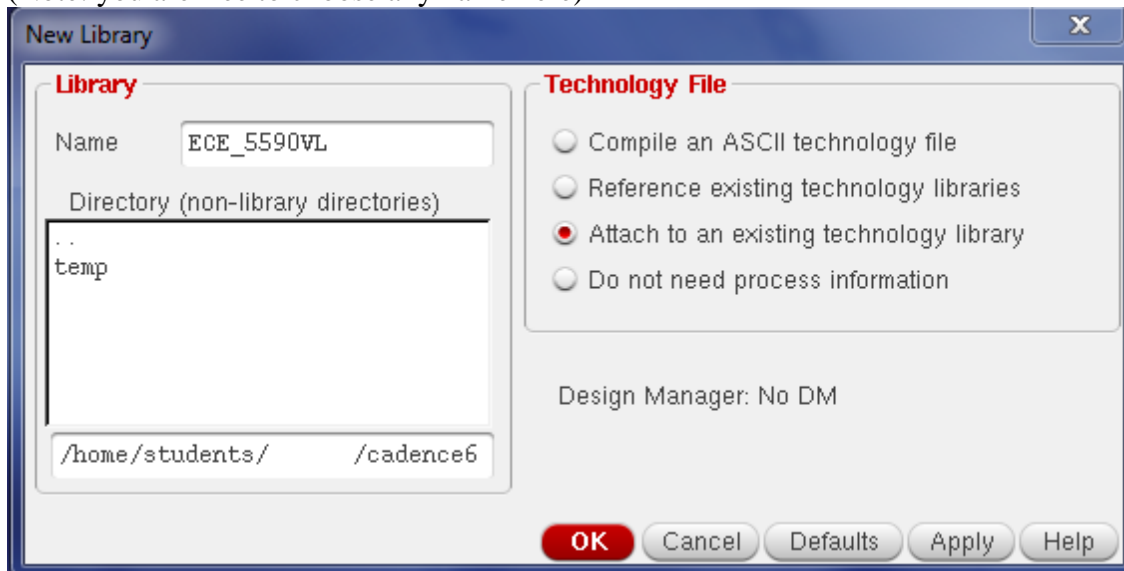
(Note: you are free to choose any name here)



 
Click on NCSU_TechLib_ami06 → ok on the library window



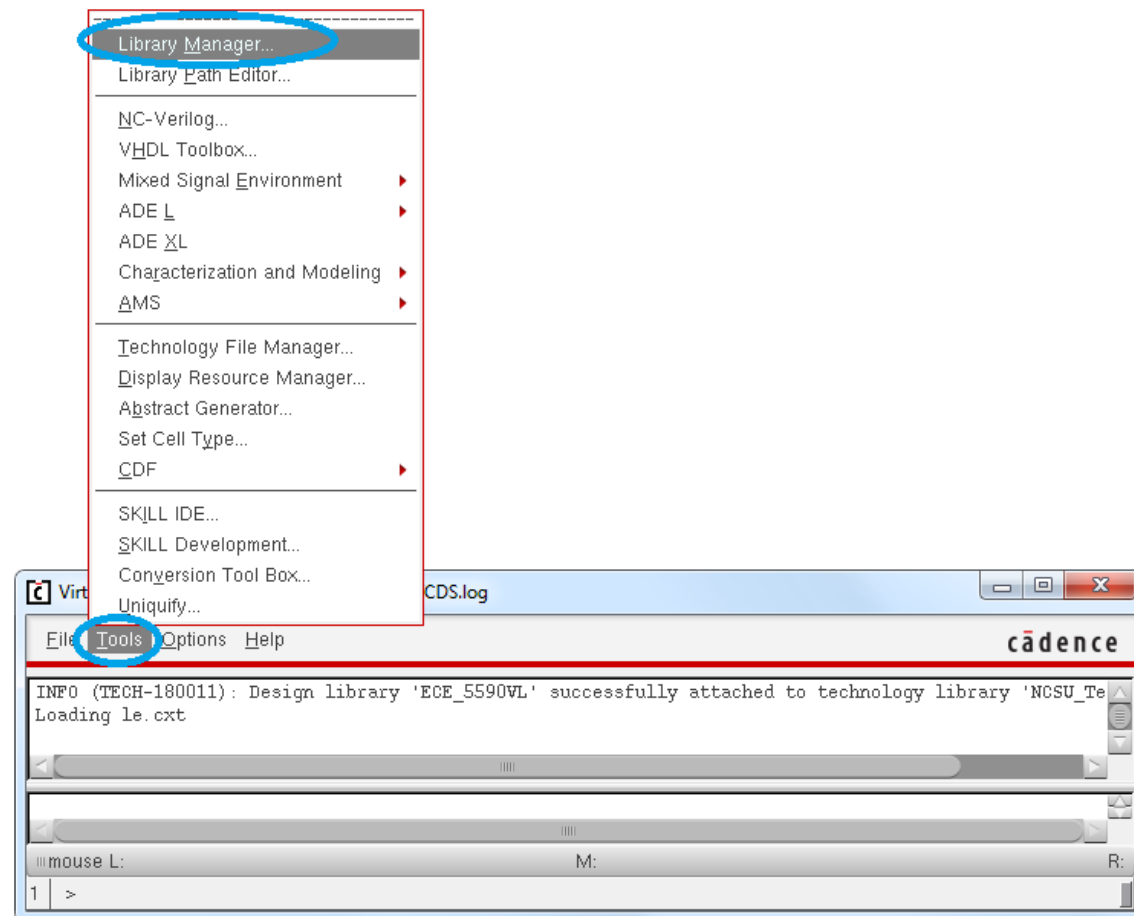
To make sure you have created the library file correctly click on Tools → Library



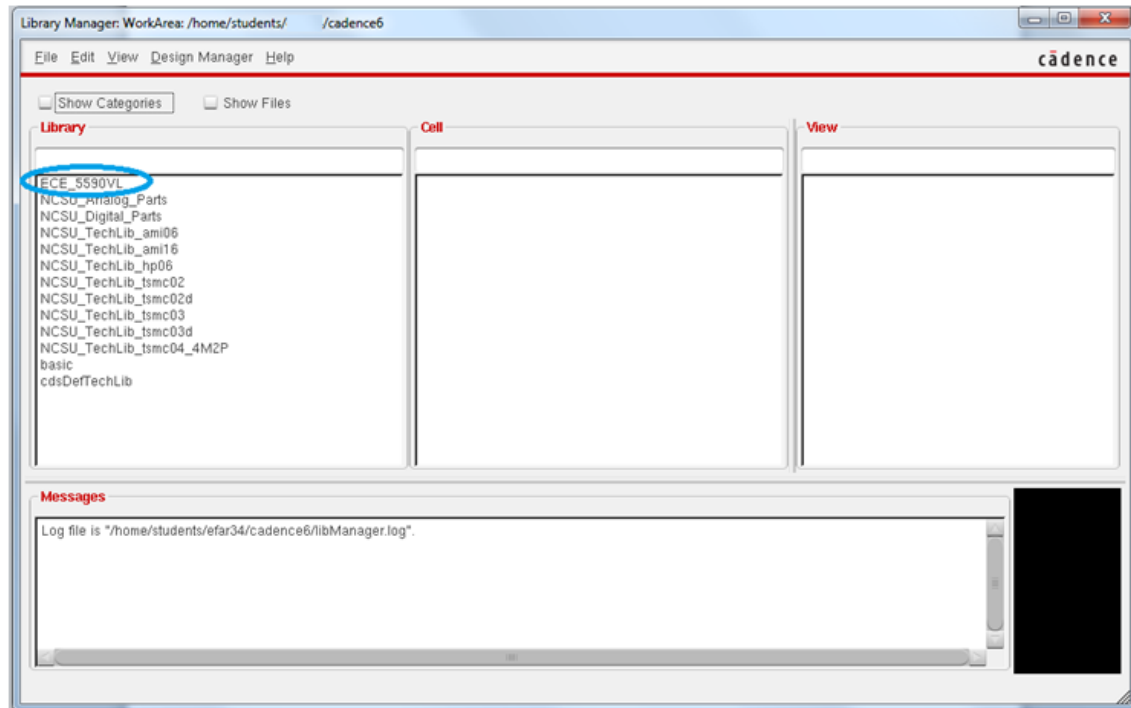
You should see your library file as shown



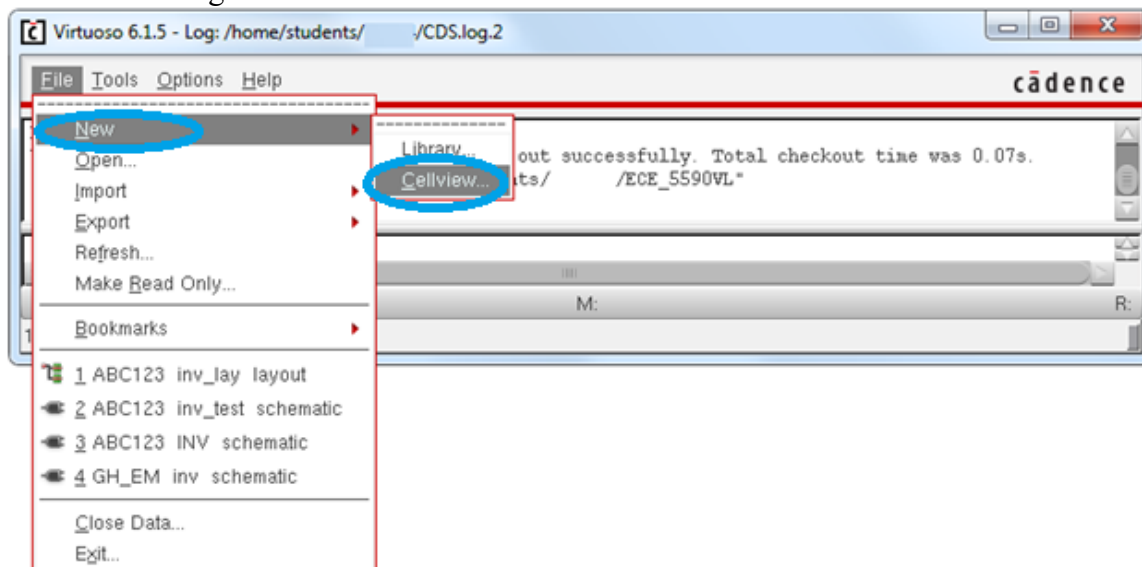
On the following window click on File → New → Cellview



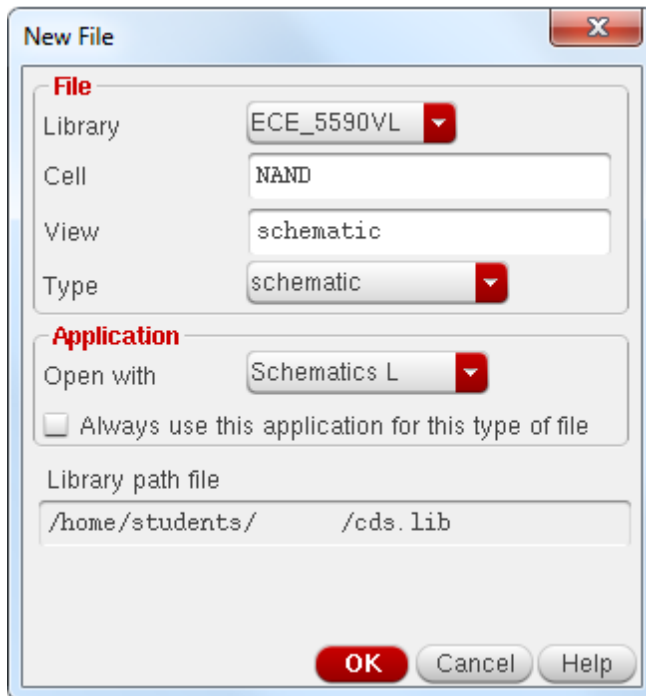
Then, on the following window type NAND for Cell file name. On the library button, scroll up and down to pick the right library name and click ok.



 Then, the following window will appear. Click **Yes**.



 At this point, you should see virtuoso schematic editor window as shown on the bottom.




Adding NMOS and PMOS Transistors


Now, we will be placing the PMOS and NMOS transistors on the schematic window editor.

To place PMOS:

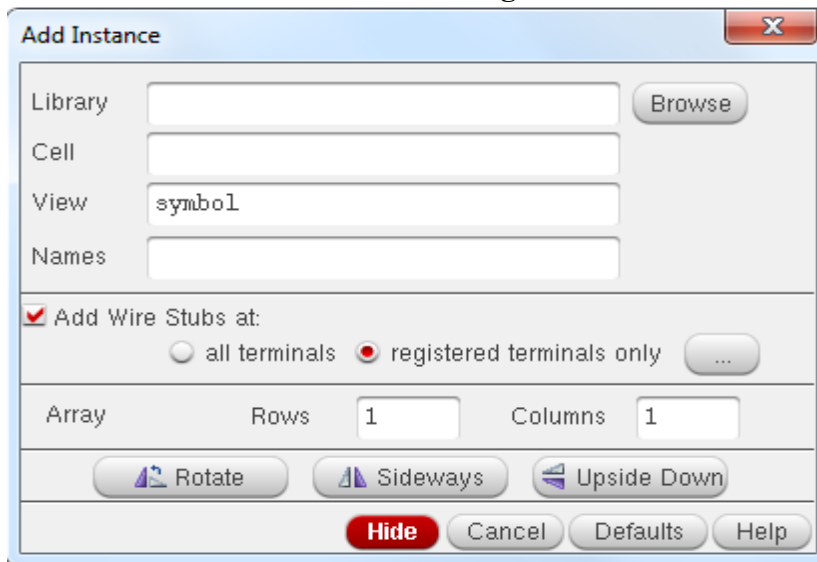
Create → Instance then the following window will come.



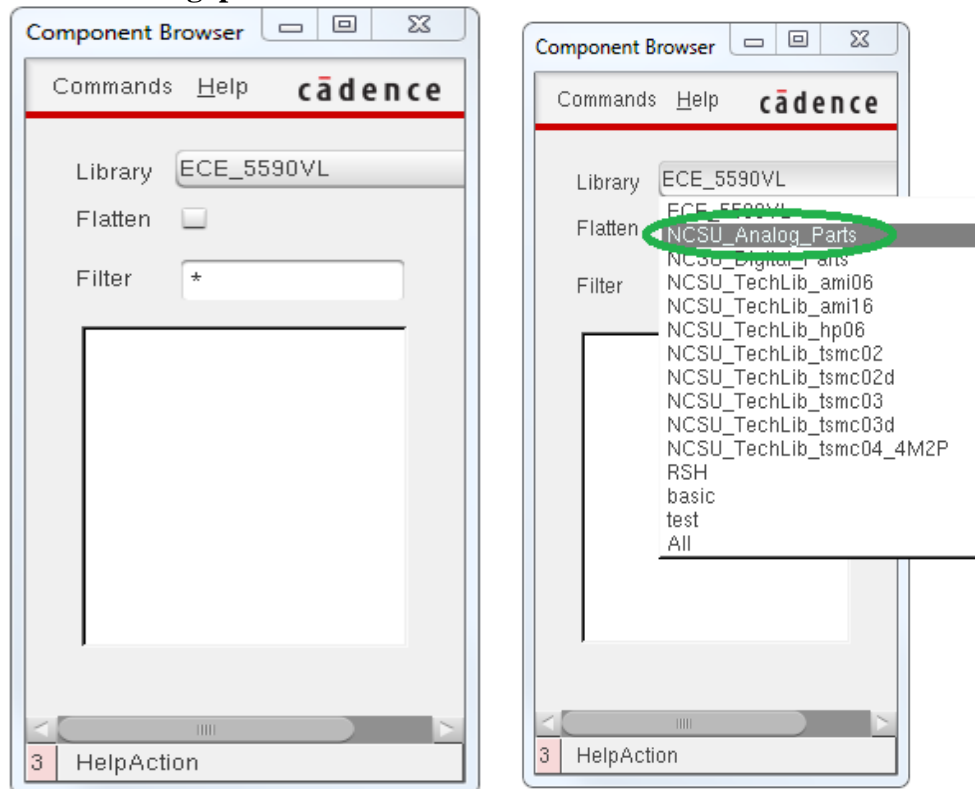When you click on **Browse** the **Component Browser** window will be opened. Select **NCSU_Analog_parts**.




Then, click on **P_Transistors → pmos**

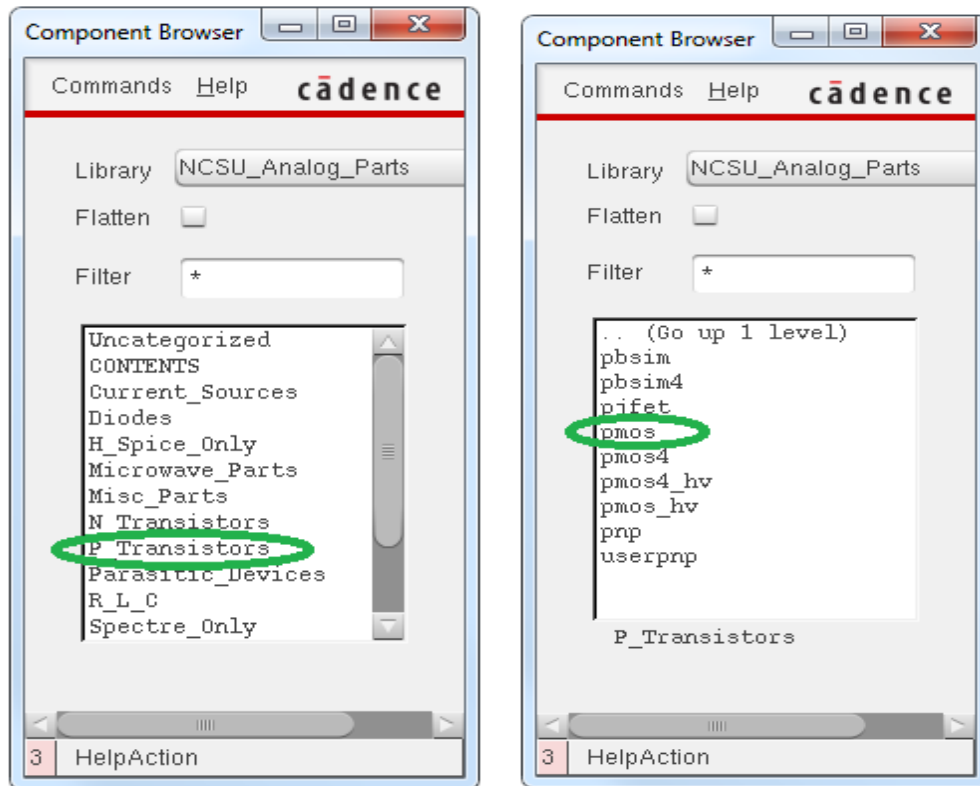



(Note: You can click on the (Go up 1 level) to go back to the previous selections)

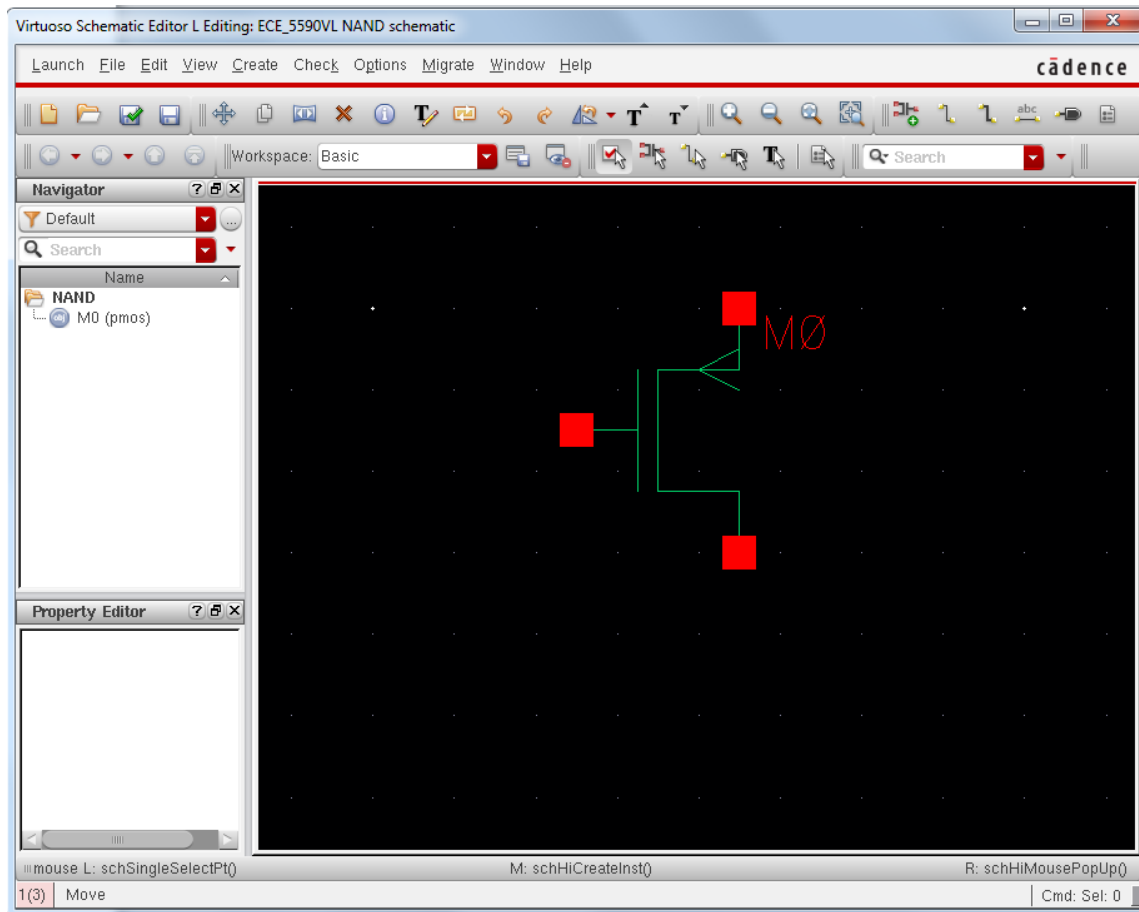When you click **Close**, the cursor will change to a transistor symbol. Place the **PMOS** on the virtuoso schematic editor window by left clicking on the mouse.



To change the characteristics of the PMOS, left click on the **PMOS** then type **q** or left click on the **PMOS** then go to **Edit** → **Properties** → **Objects**. The following window should appear

On the Edit Object Properties window enter the values for PMOS shown here and click

 Add Instance@kc-csrv-sce-tux01.kc.umkc.edu 

Library

Cell

View

Names

☒ Add Wire Stubs at:
☐ all terminals ☒ registered terminals only

Array Rows Columns

Model name

Model Type ☒ system ☐ user

Multiplier

Fingers

Width (grid units)

Width

Width (minimum)

Length (grid units)

Length

Length (minimum)

Drain diffusion area

Source diffusion area

Drain diffusion perimeter

Source diffusion perimeter

Drain diffusion res squares


Source diffusion res squares

Virtuoso-XL layout cell

Drain diffusion length

Source diffusion length

Temp rise from ambient

Estimated operating region 

Place one more PMOS and then repeat the same process for NMOS

Add Instance@kc-csrv-sce-tux01.kc.umkc.edu

Library:

Cell:

View:

Names:

☒ Add Wire Stubs at:

☐ all terminals ☒ registered terminals only

Array: Rows Columns

Model name:

Model Type: ☒ system ☐ user

Multiplier:

Fingers:

Width (grid units):

Width:

Width (minimum):

Length (grid units):

Length:

Length (minimum):

Drain diffusion area:

Source diffusion area:

Drain diffusion perimeter:

Source diffusion perimeter:

Drain diffusion res squares:

Source diffusion res squares:

Virtuoso-XL layout cell:


Drain diffusion length:

Source diffusion length:

Temp rise from ambient:

Estimated operating region:

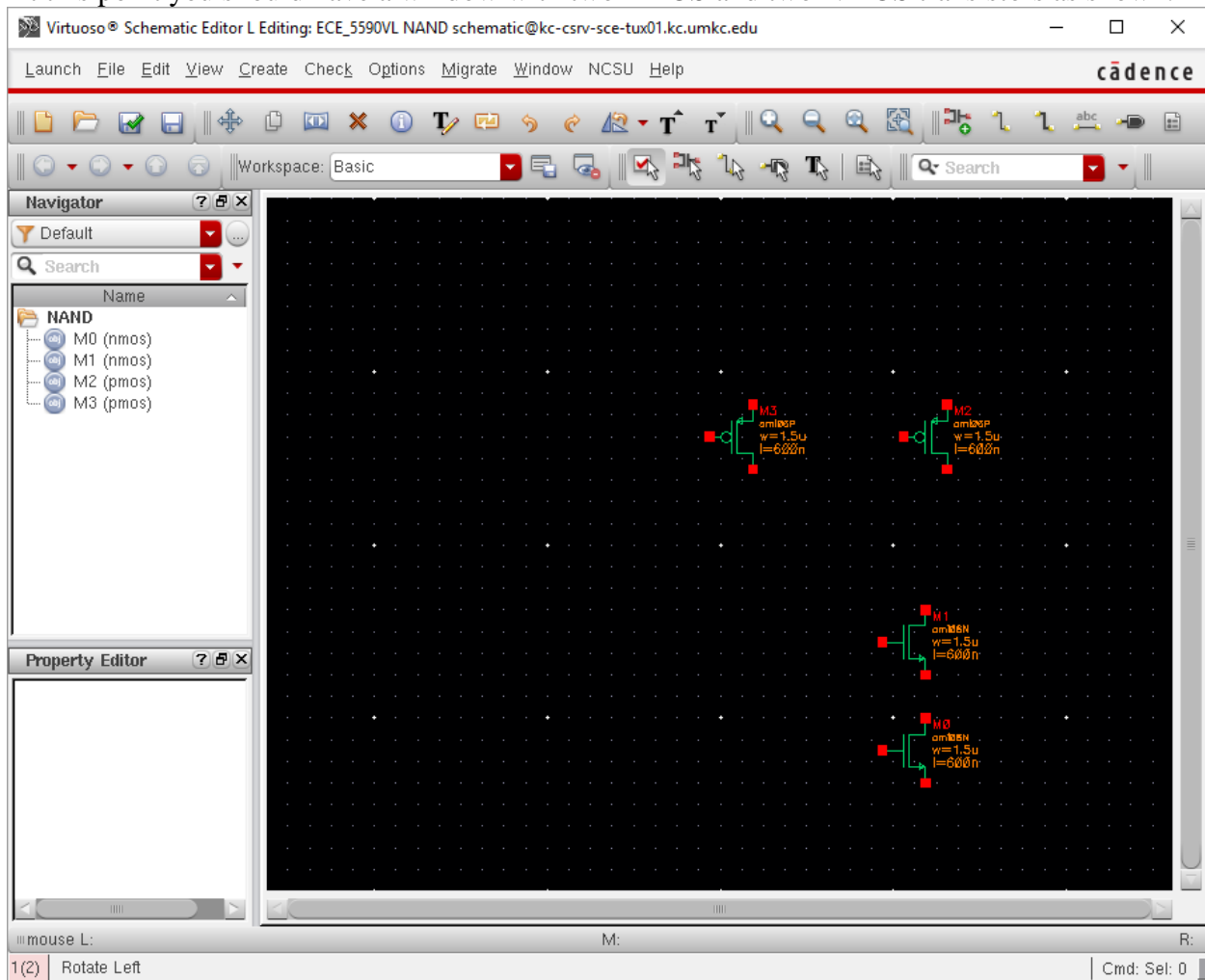At this point you should have a window with two PMOS and two NMOS transistors as shown.



Now select and place the following objects on the window:

Create → Instance → Browse

1- NCSU_Analog_parts → Supply_Nets → vdd

2- NCSU_Analog_parts → Supply_Nets → gnd


3- NCSU_Analog_parts → Voltage_Sources → vdc

i. left click on vdc → q → DC voltage **5v V**

4- NCSU_Analog_parts → Voltage_Sources → vpulse

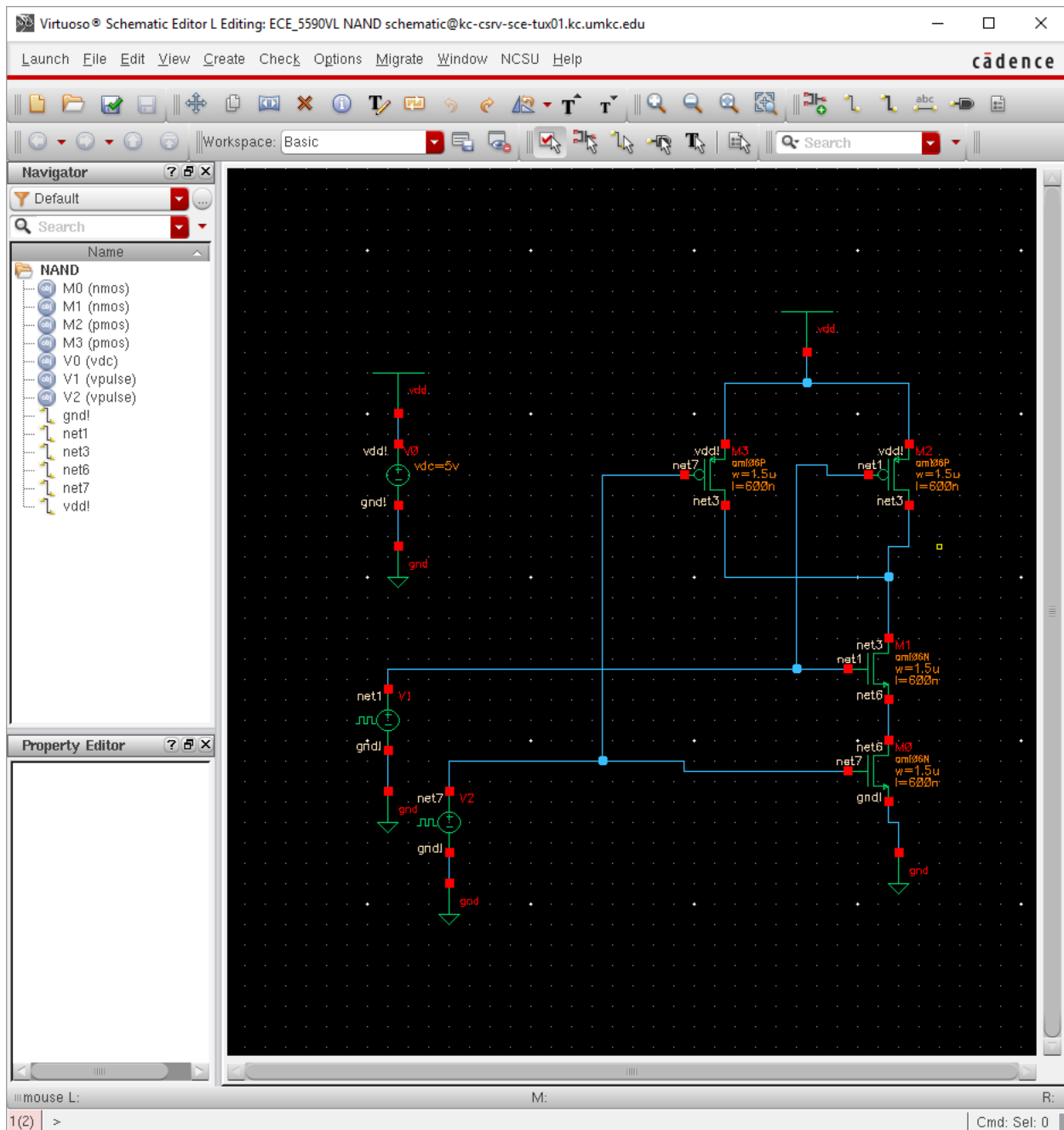i. place two vpulses

You should connect all the components by wire. To connect the one terminal of component to another click the red square box OR press “w” then under your mouse cursor a small wire will come and then connect the components like shown below.



In order to observe the output we need to configure the timing of the Vpulse for each input. Click on the Vpulse and then change its properties by pressing “q”

ECE – 5590VL/ ECE-401VL Introduction to VLSI Laboratory Manual

Edit Object Properties@kc-csrv-sce-tux01.kc.umkc.edu

Apply To
only current
instance
Show
system
user
CDF

Browse
Reset Instance Labels Display

Property	Value	Display
Library Name	NCSU_Analog_Parts	off
Cell Name	vpulse	off
View Name	symbol	off
Instance Name	V1	off

Add
Delete
Modify

User Property	Master Value	Local Value	Display
Ivsignore	TRUE		off

CDF Parameter	Value	Display
AC magnitude		off
AC phase		off
Voltage 1	0 V	off
Voltage 2	5v V	off
Delay time	30n s	off
Rise time	110p s	off
Fall time	110p s	off
Pulse width	60n s	off
Period	120n s	off
DC voltage		off
Noise file name		off
Number of noise/freq pairs	0	off
Temperature coefficient 1		off
Temperature coefficient 2		off
Nominal temperature		off

OK
Cancel
Apply
Defaults
Previous
Next
Help

Edit Object Properties@kc-csrv-sce-tux01.kc.umkc.edu

Apply To
only current
instance
Show
system
user
CDF

Browse
Reset Instance Labels Display

Property	Value	Display
Library Name	NCSU_Analog_Parts	off
Cell Name	vpulse	off
View Name	symbol	off
Instance Name	V2	off


Add
Delete
Modify

User Property	Master Value	Local Value	Display
Ivsignore	TRUE		off


CDF Parameter	Value	Display
AC magnitude		off
AC phase		off
Voltage 1	0 V	off
Voltage 2	5v V	off
Delay time	60n s	off
Rise time	110p s	off
Fall time	110p s	off
Pulse width	60n s	off
Period	120n s	off
DC voltage		off
Noise file name		off
Number of noise/freq pairs	0	off
Temperature coefficient 1		off
Temperature coefficient 2		off
Nominal temperature		off

OK
Cancel
Apply
Defaults
Previous
Next
Help


Click on Create → Wire Name

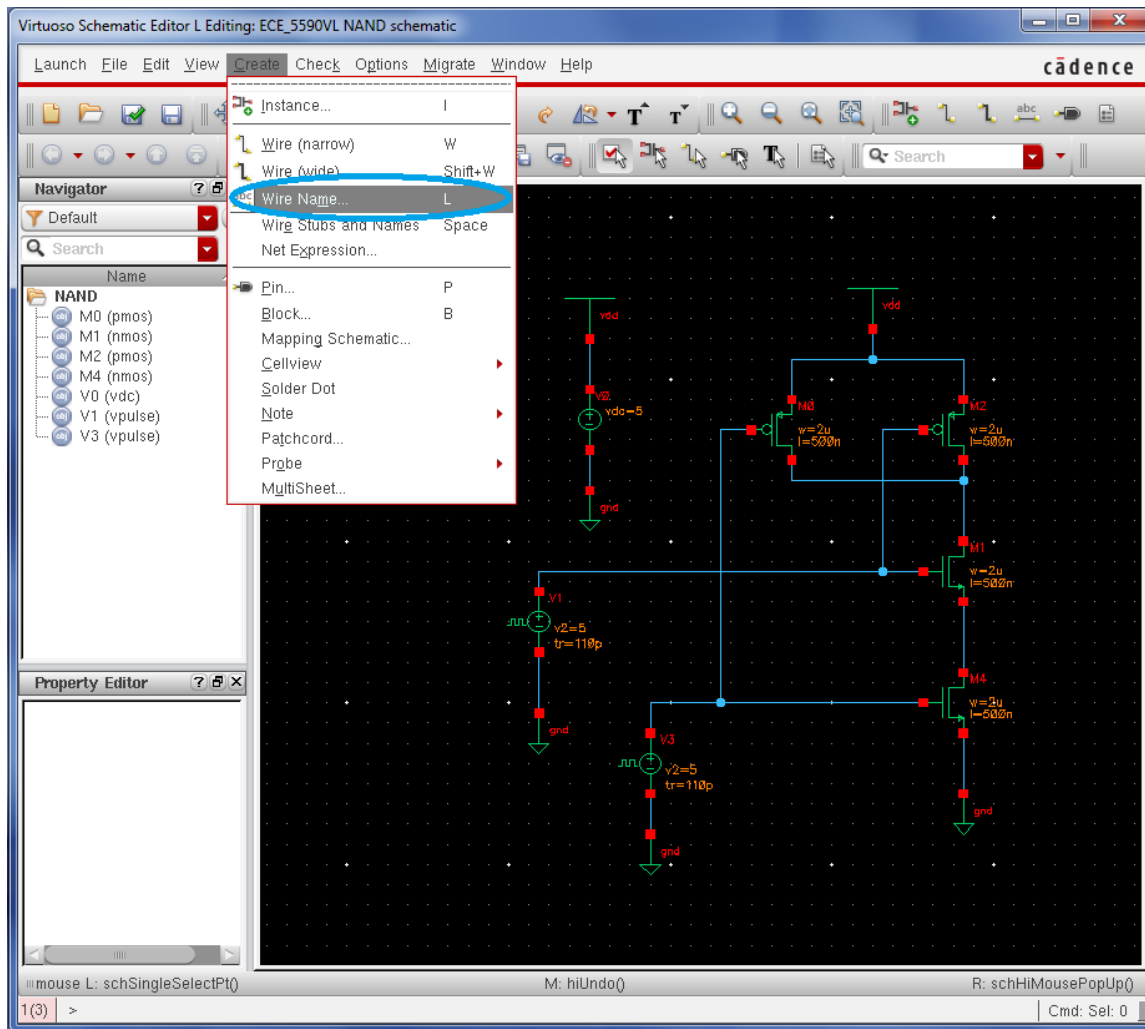


Add Wire Name window will appear

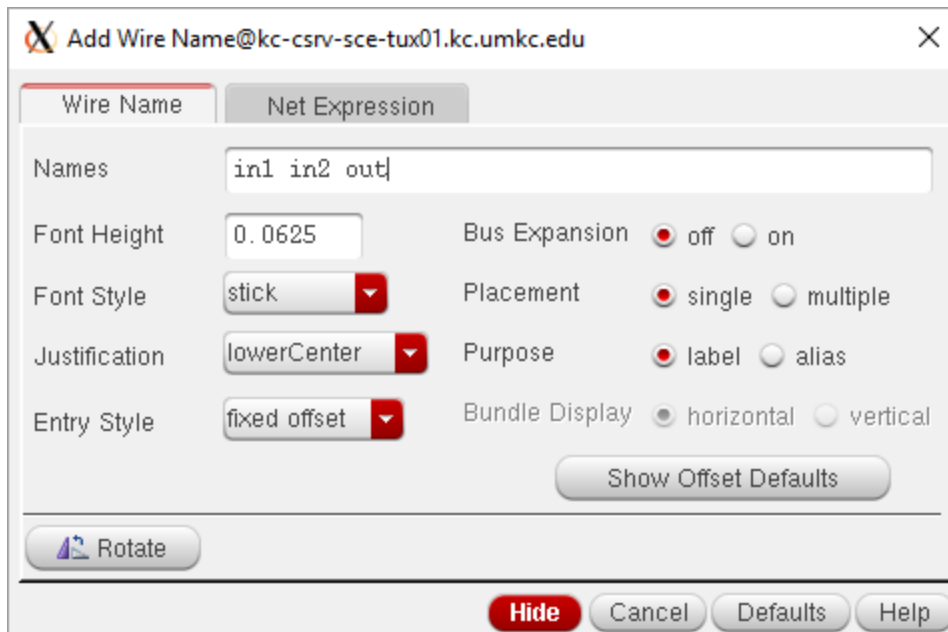

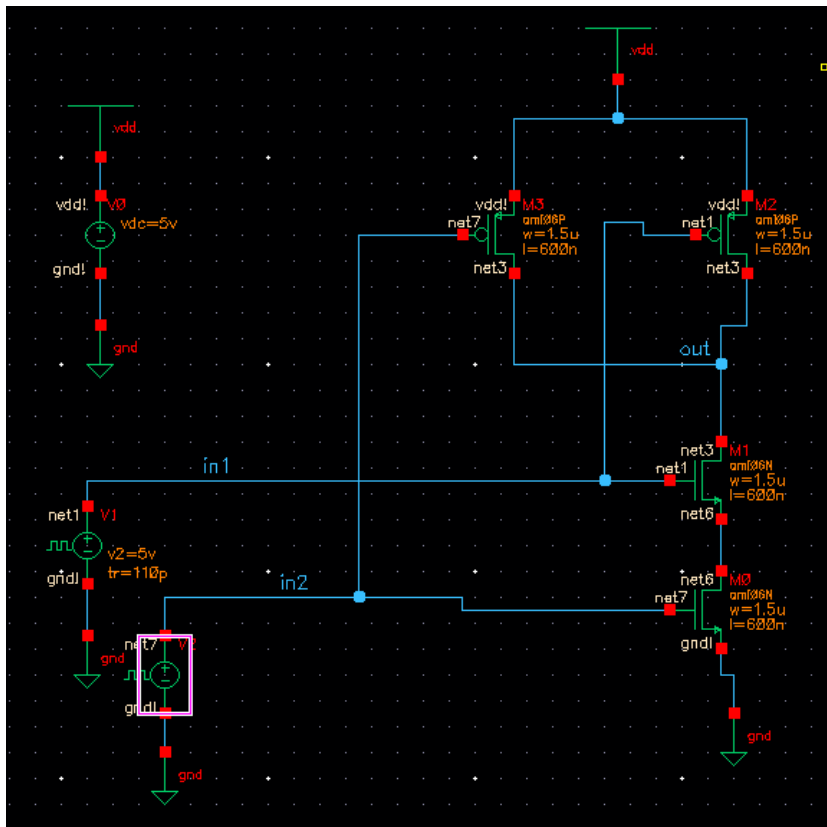Write in1 in2 out in the names and then click on the schematic to name the wires respectively.



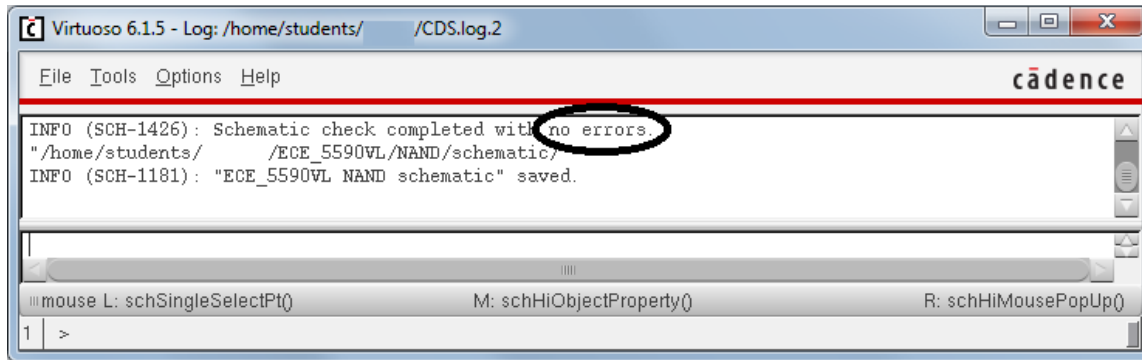
If you make a mistake you can always use **u** to undo it. Now click **Check and Save** button. Then you should see the virtuoso window. Make sure your design is free of error.




Simulation of your Circuit

We are now ready to do simulation

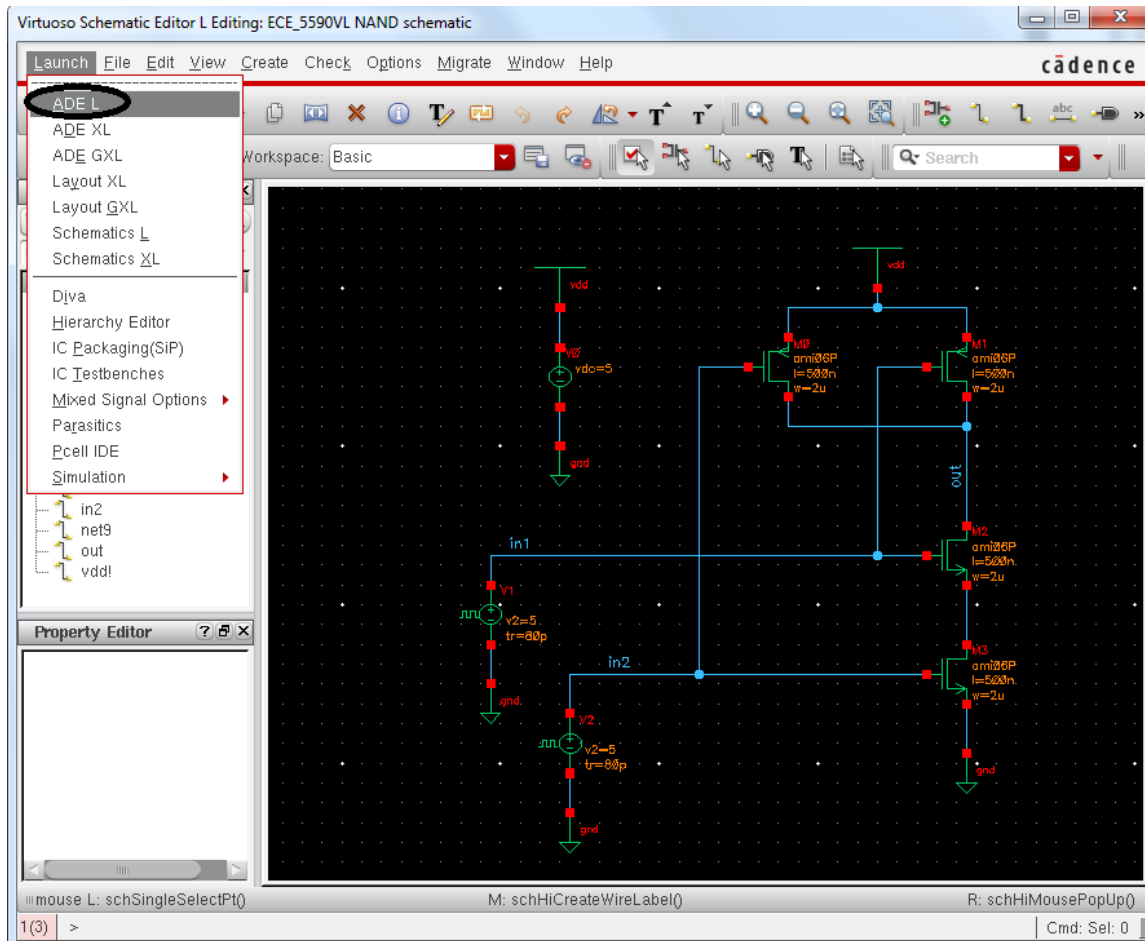
From Virtuoso Schematic Editor click on **Launch** → **ADE L**




The following window should appear.

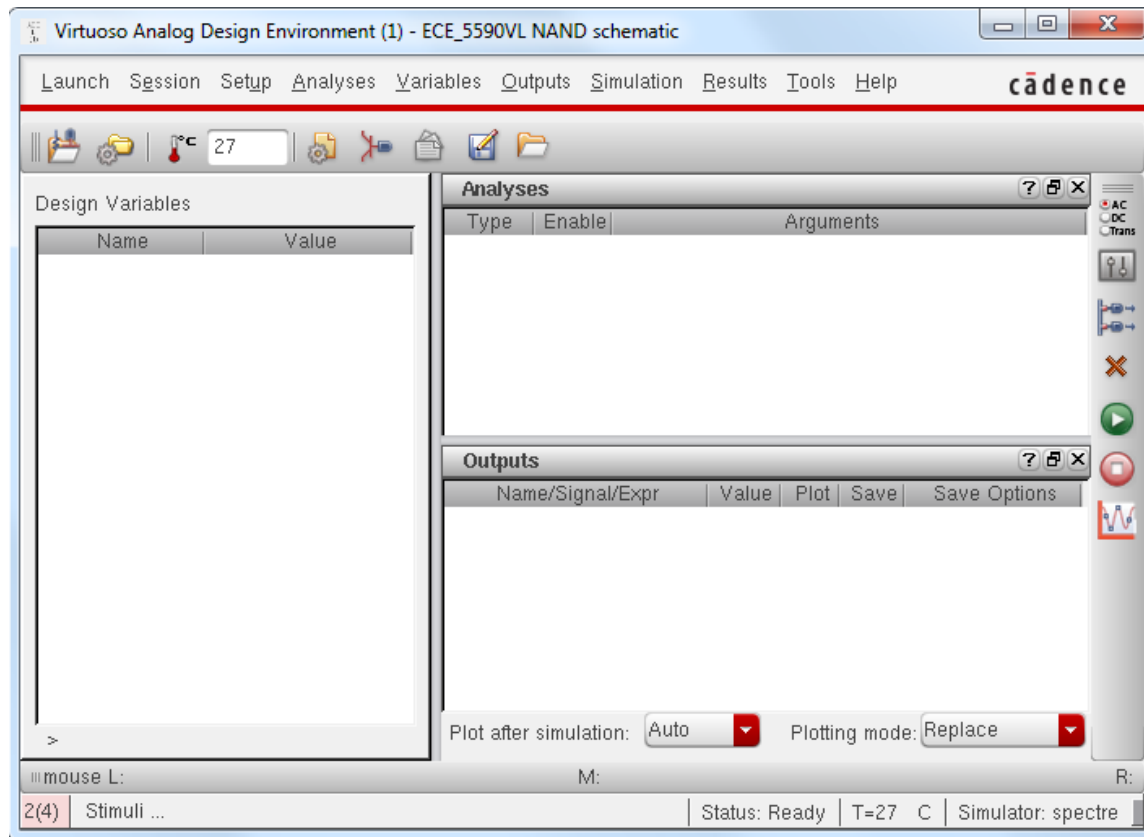

 
If you see an error window click **Yes**.



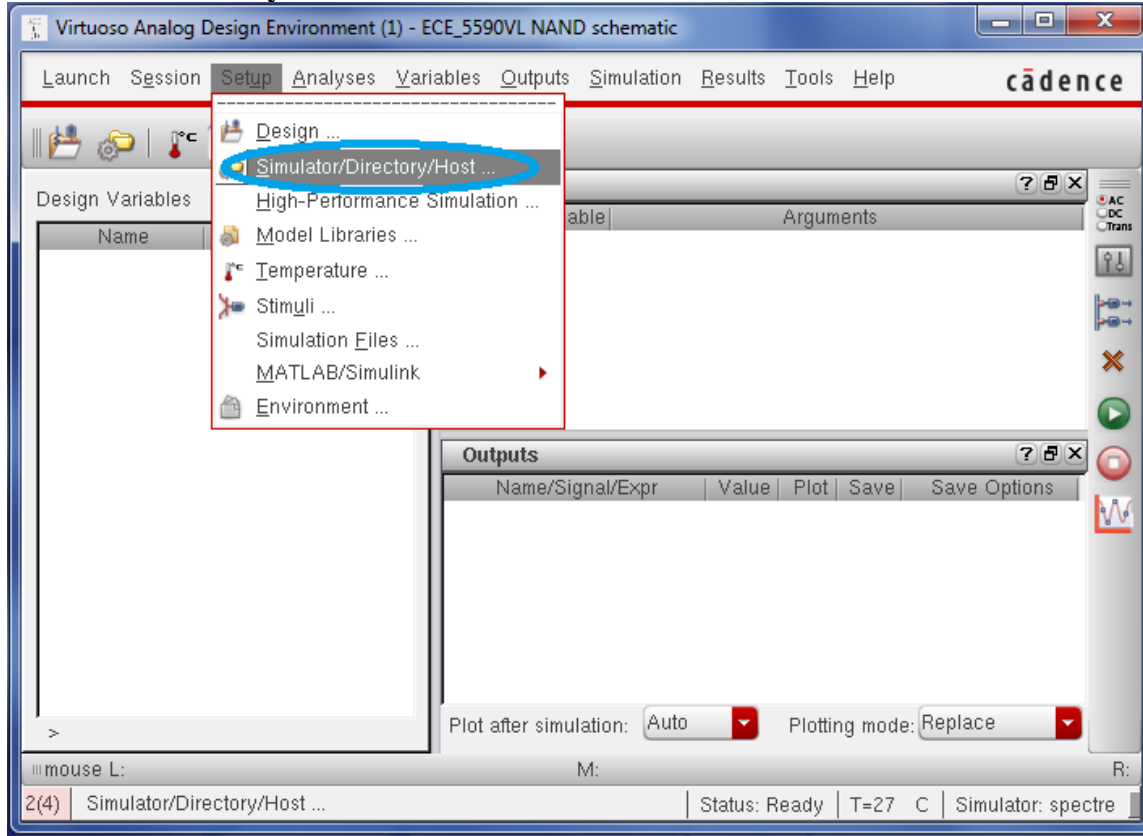On the virtuoso analog design environment window click on **Setup** → **Simulator/Directory/Host**




The following window should appear.

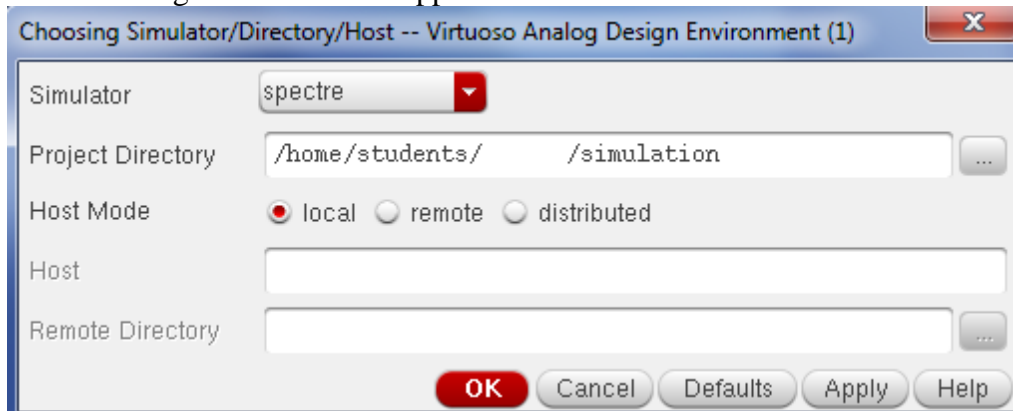


In the above window scroll up and down and select **spectre** under **Simulator** selection and click **ok**.

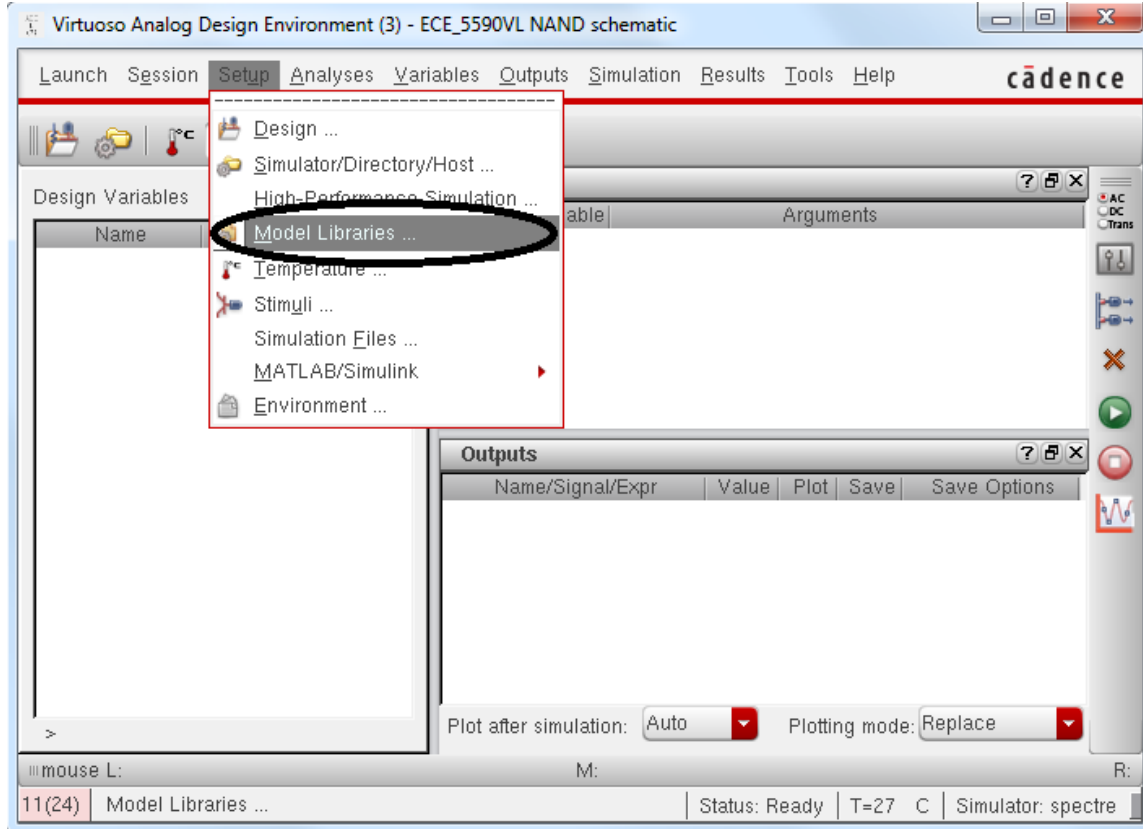
Next, on the **Virtuoso Analog Design Environment** window click on **Setup** → **Model Libraries**



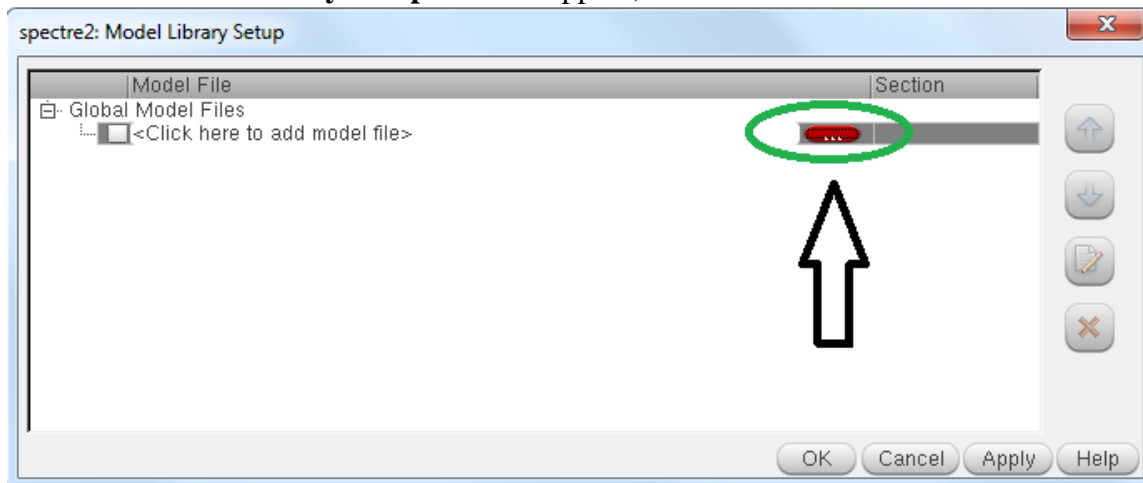
When the **Model Library Setup** window appear, click at the location shown below.



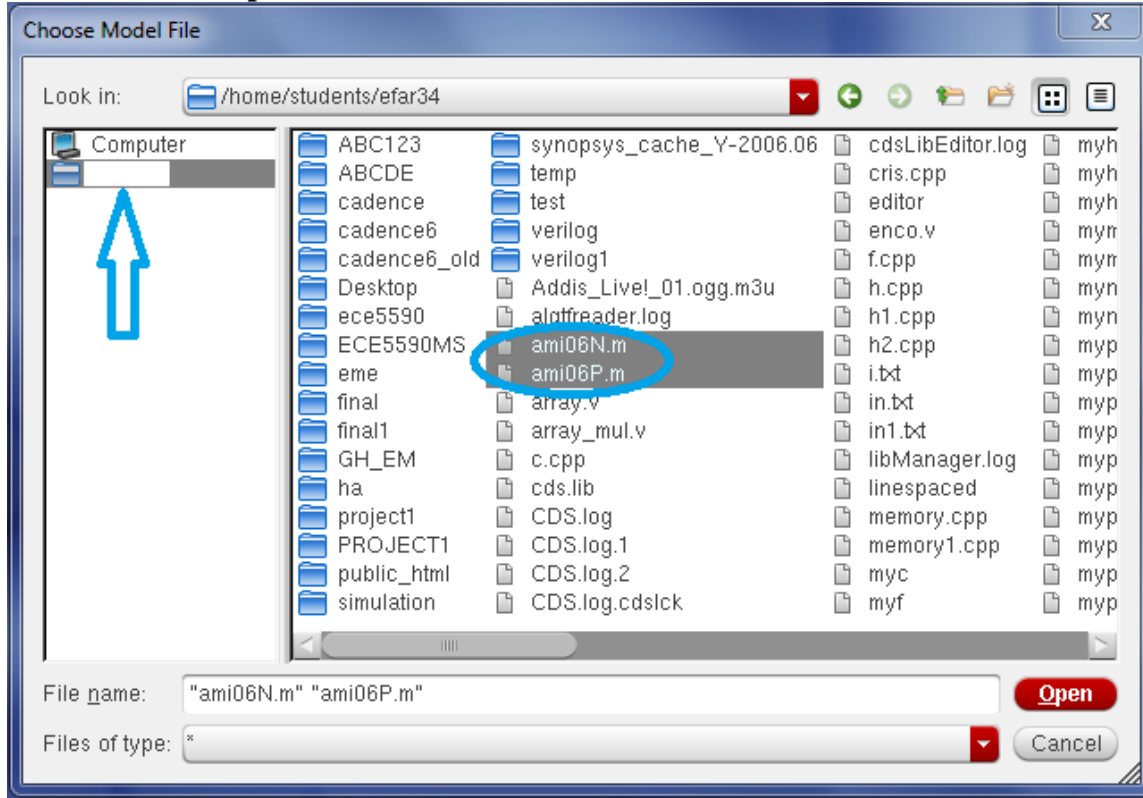
On the choose model file window, first click on your user name then, select the libraries as shown and click **Open**



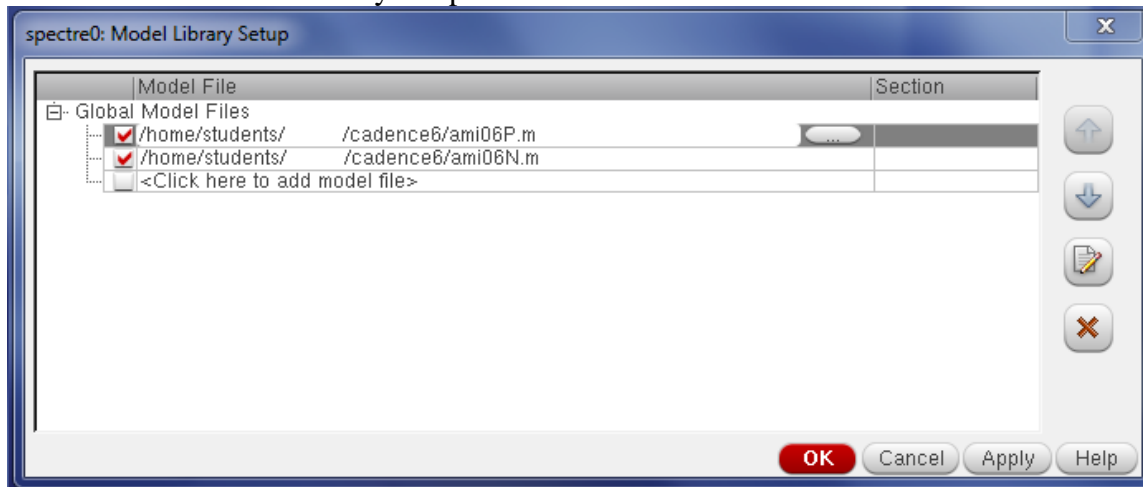Click **ok** on the Model library setup window.




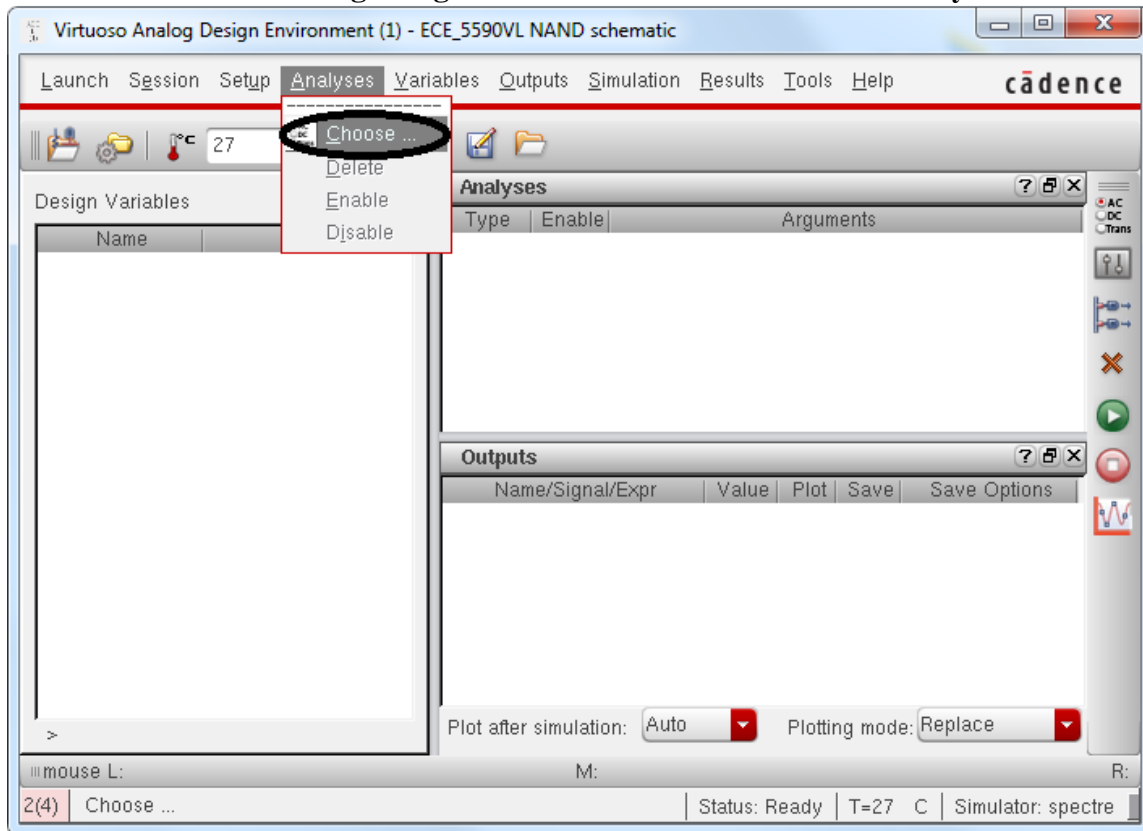Under the **Virtuoso Analog Design Environment** window click on **Analyses** → **Choose**




When

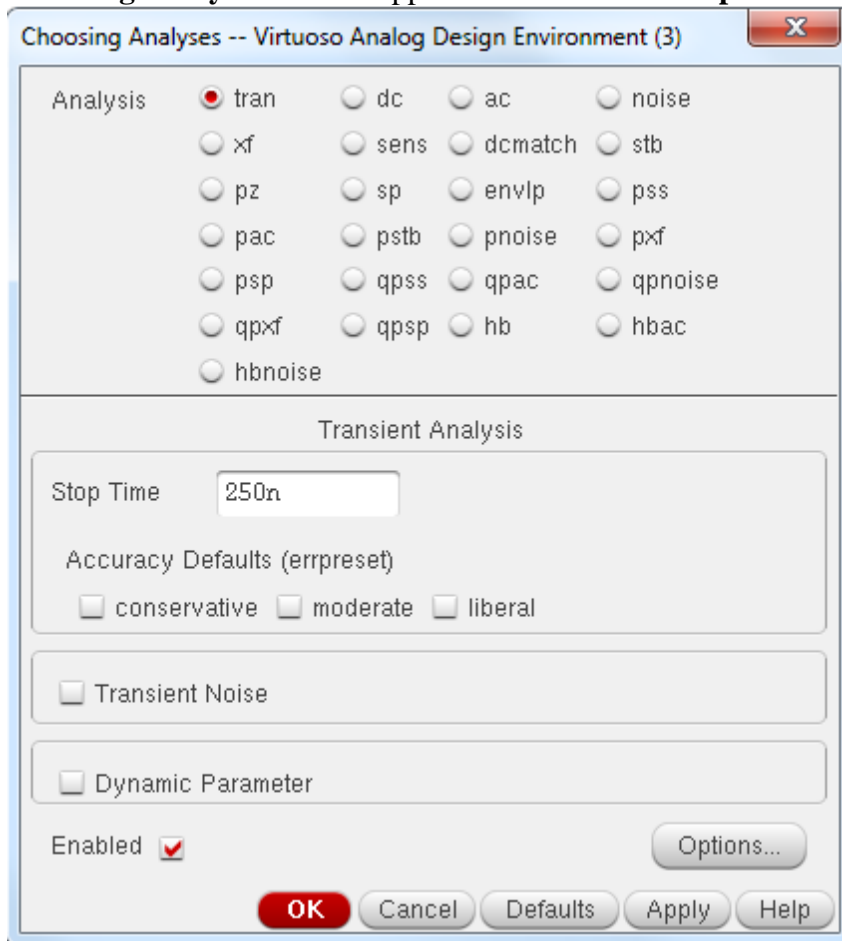
Choosing Analysis window appear enter **250ns** for **Stop Time** and click **ok**.



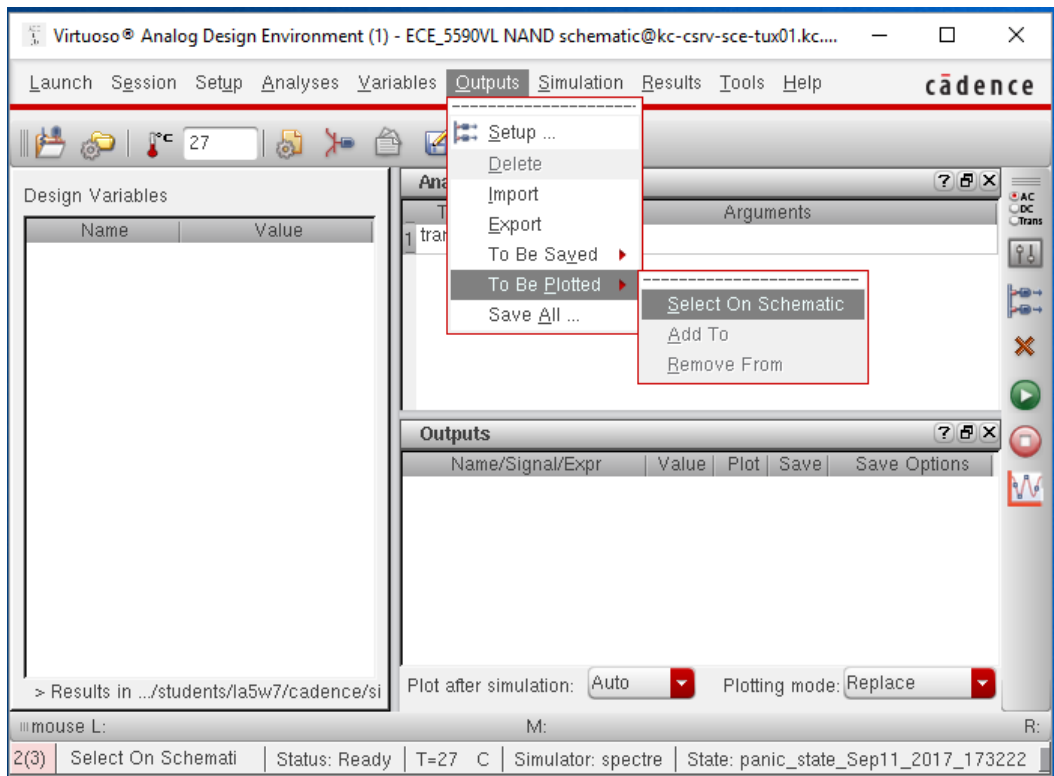To Select the signals for input and output do the following




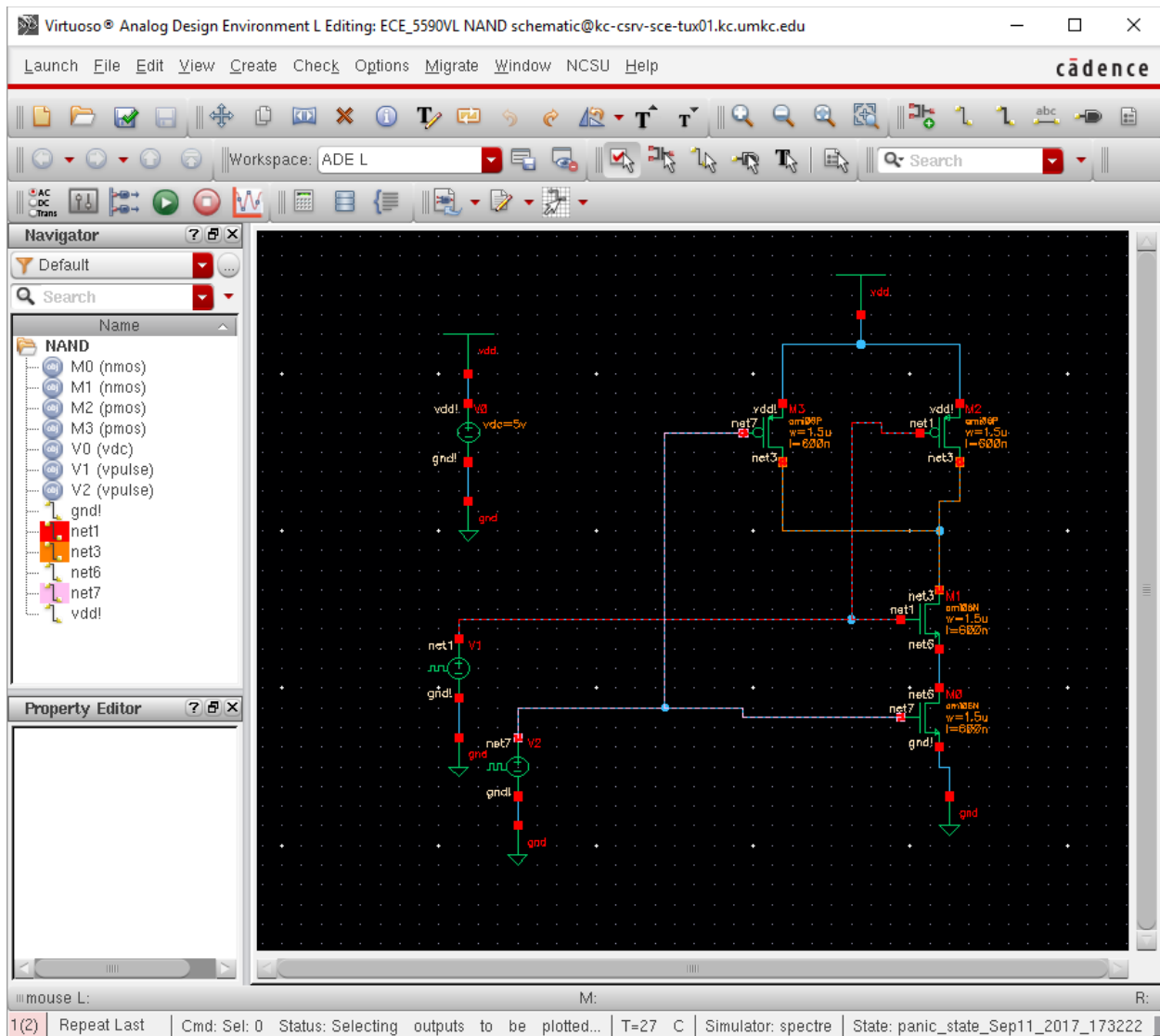Now select the signals from the schematic




On the **Virtuoso Analog Design Environment** window **Simulation → Run**

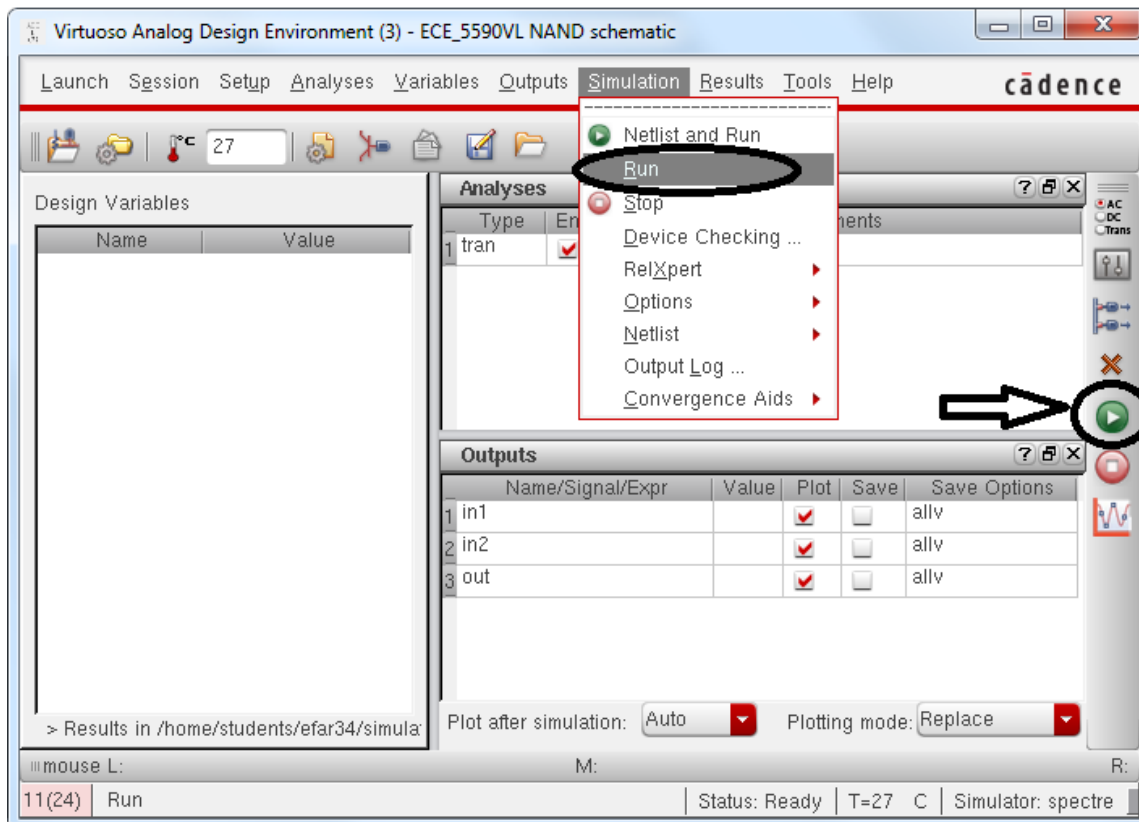
(Note: you could also click on the green run button at the right side of the window)



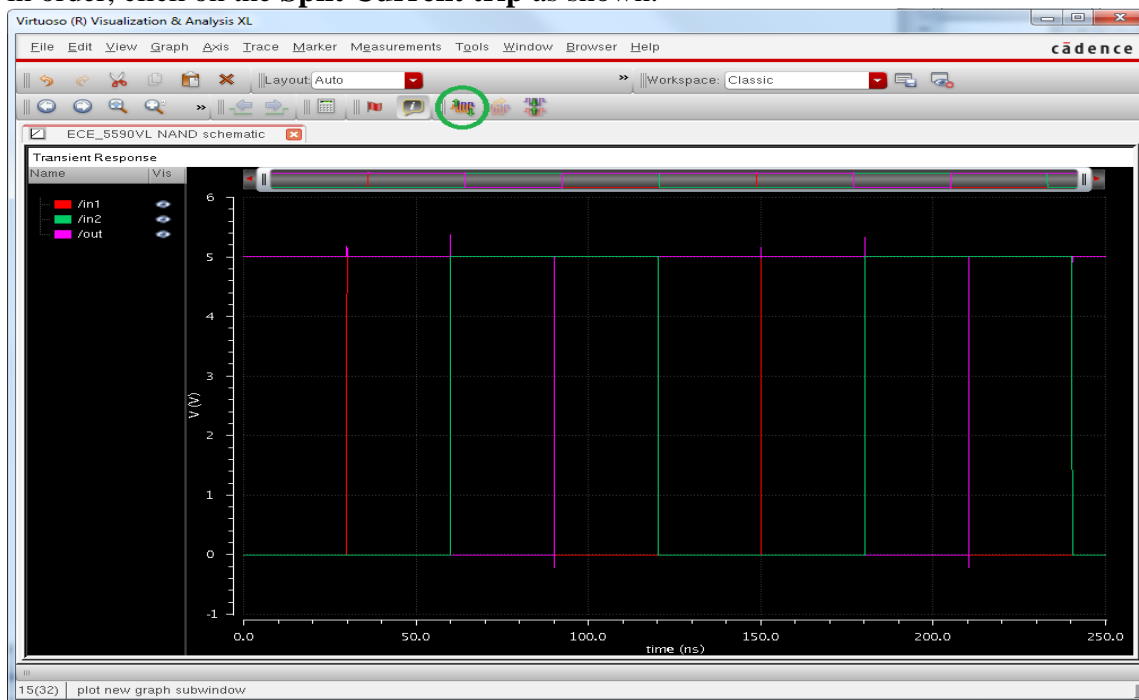
Now, you should see **Virtuoso Visualization & Analysis window**. To see the inputs and output in order, click on the **Split Current trip** as shown.



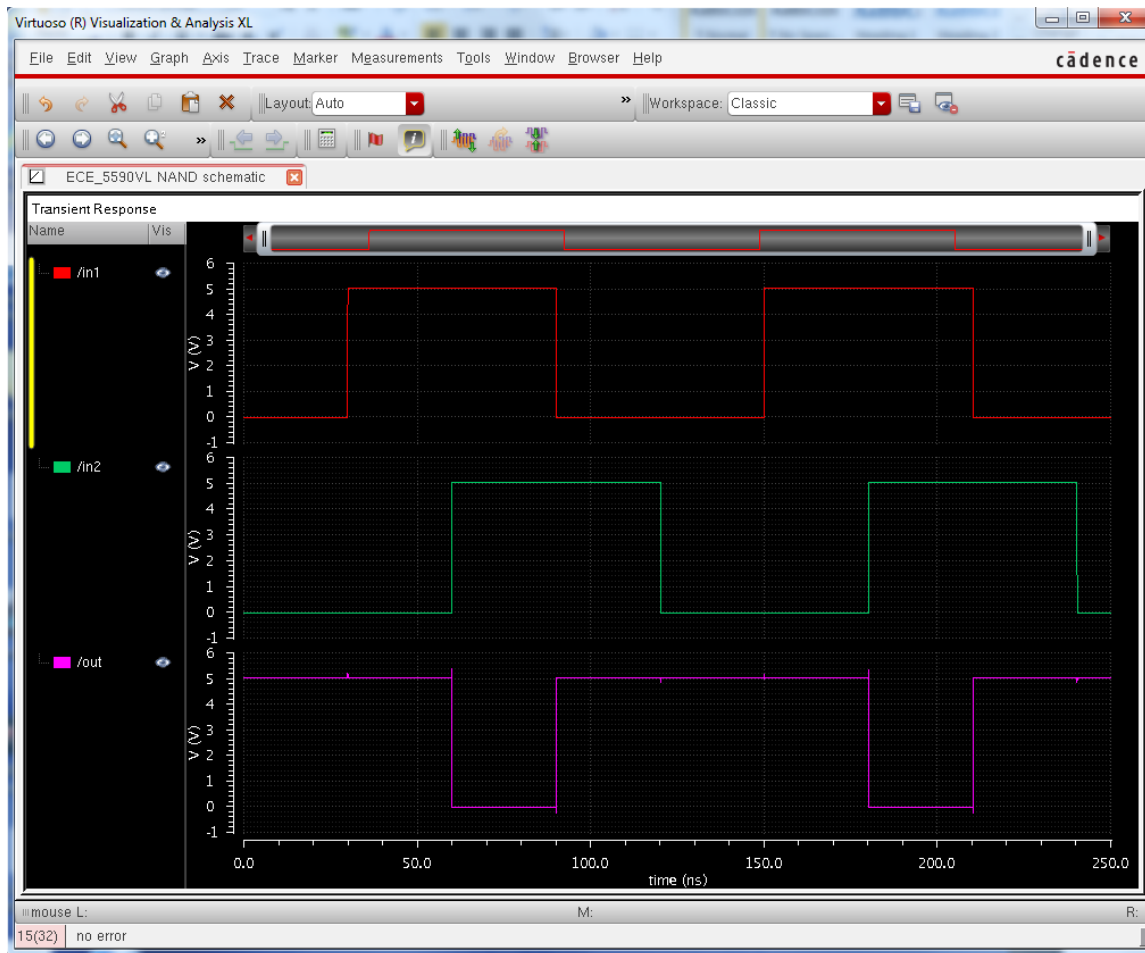At this point the **Virtuoso Visualization & Analysis** window should look as follow.



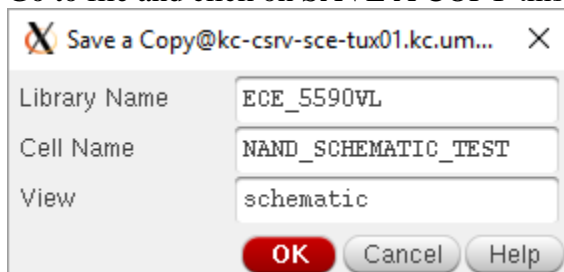Go to file and click on SAVE A COPY this file as “NAND_SCHEMATIC_TEST”




Creating the AND symbol

Close the things. Open the virtuoso again and open the file NAND.

We are now ready to create a NAND symbol

Even though our design is done, we will add few more things to it to make it better. Also, we will create a **NAND symbol**.

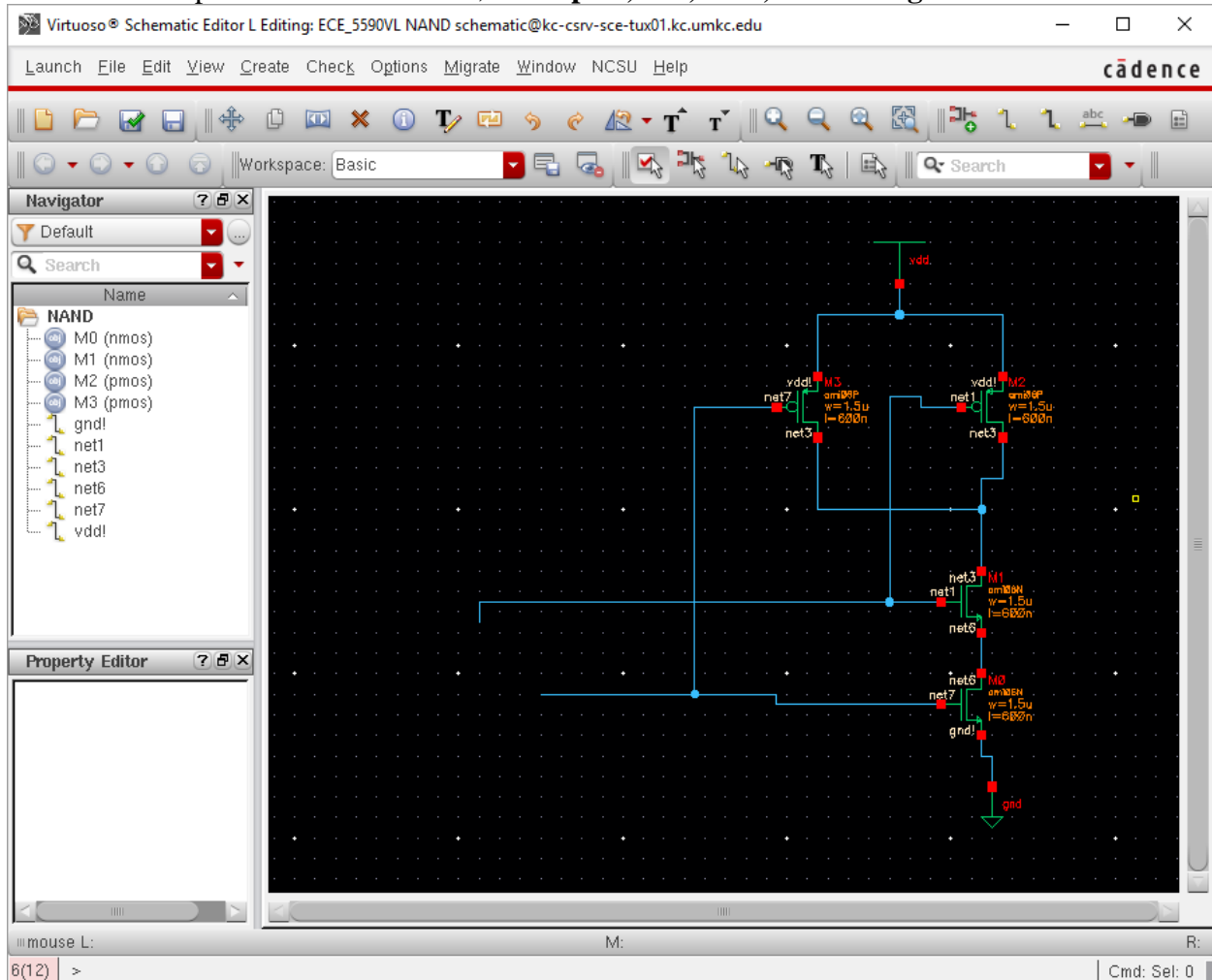
Now go back to **Virtuoso Schematic Editor** window and delete all the input voltages and associated components. Which means, both **vplus**, **vdc**, **vidd**, and **three gnd** as shown below.




Note: to delete an object you have few options:

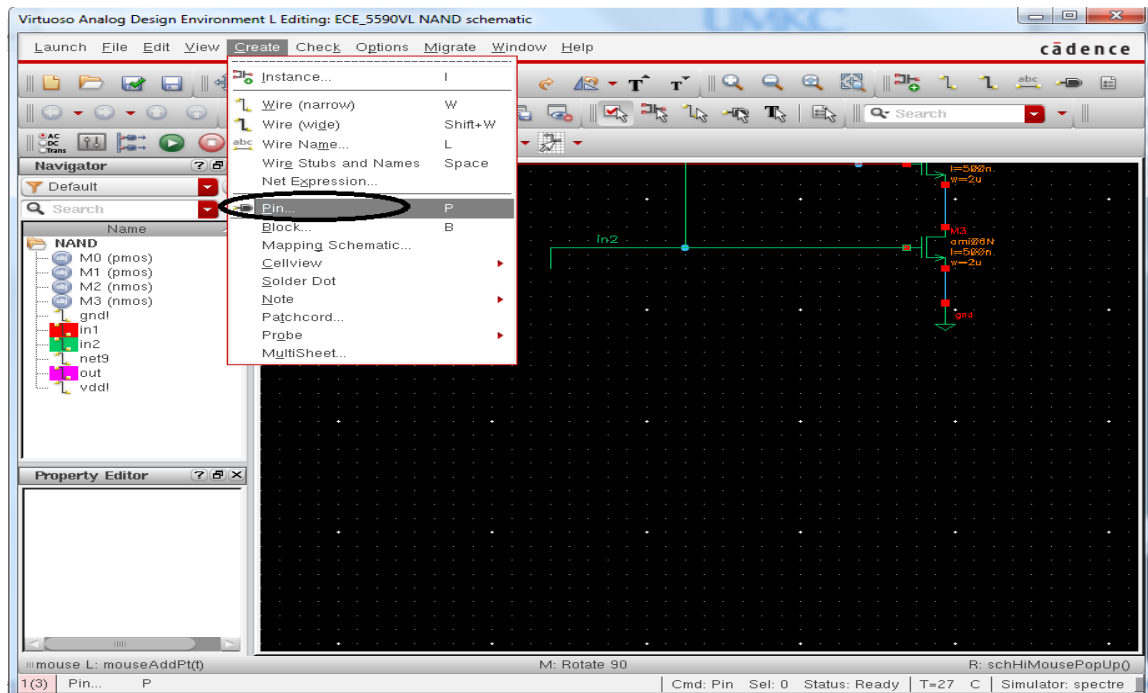1. You could select on the object and tap on delete key on the keyboard
2. You could select the object and use X button from the selection options
3. You could select the object and right click on it and then click on delete


Now we will add pins to our inputs and output. Click on **create** → **pin**



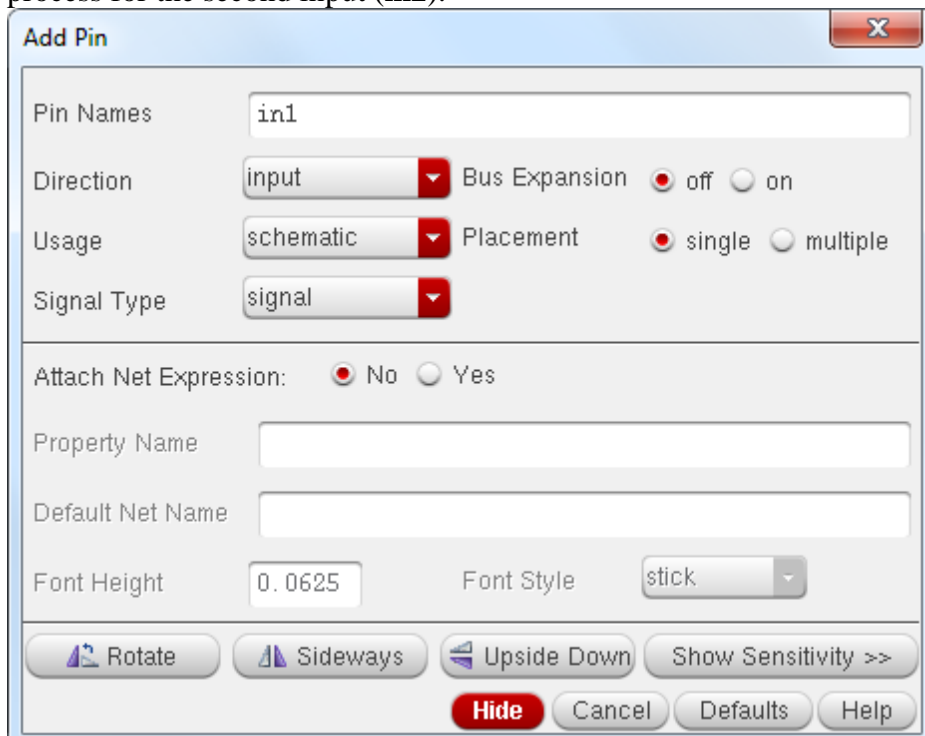
On the **Add Pin** window, under the **Pin Names** space type **in1** and chose **input** from the **Direction** selection options and click on **Hide** to place it on the window. Repeat the same process for the second input (**in2**).



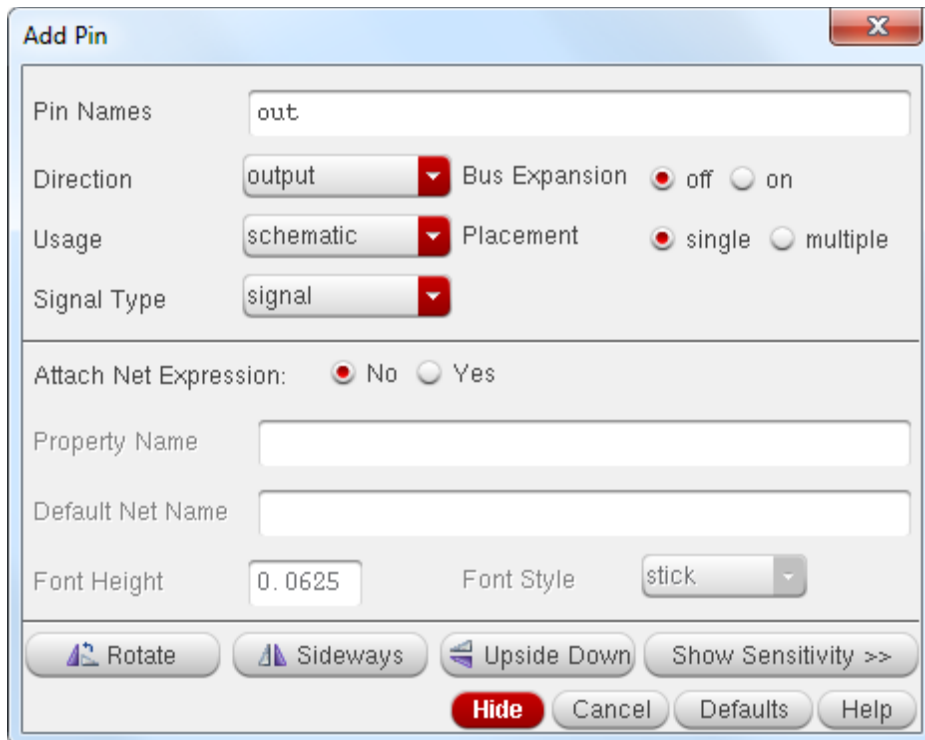
Follow the same procedure and type **out** for the output. Make sure to change the **Direction** to **output**.



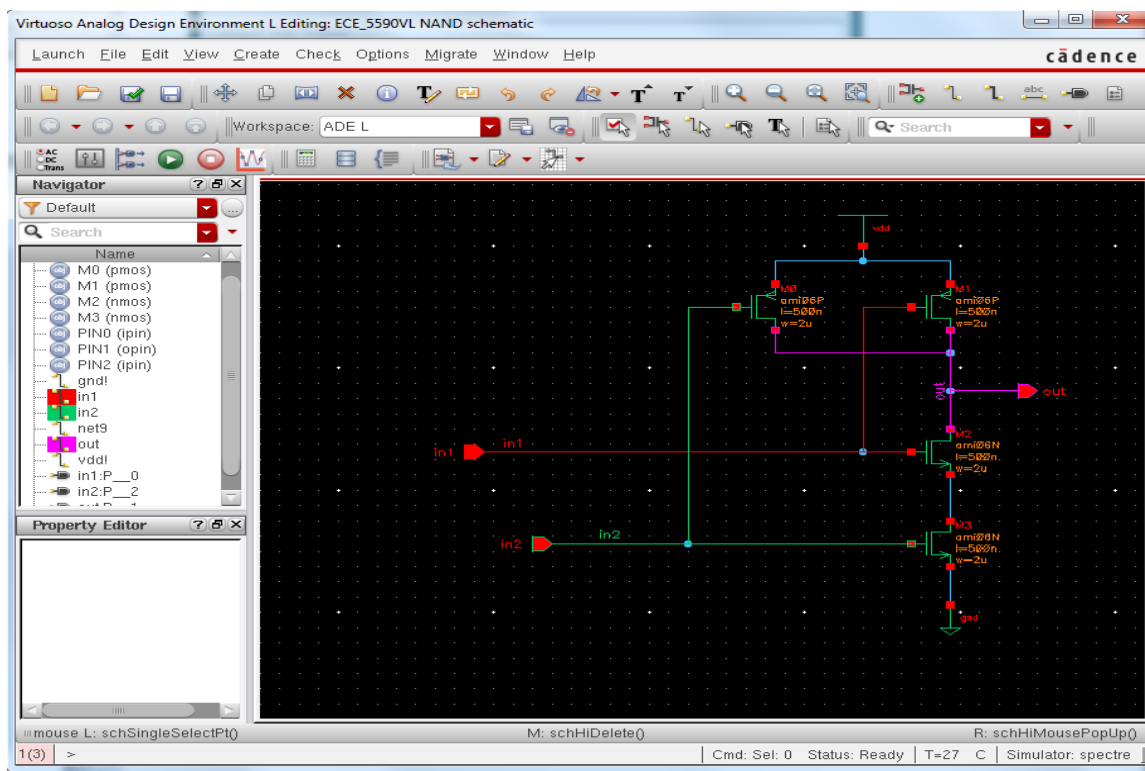
At this point, the **Virtuoso Schematic Editor** window should look as follow. Click on check and save button to verify your design. If you don't have any errors, proceed to the next steps in creating the NAND symbol.



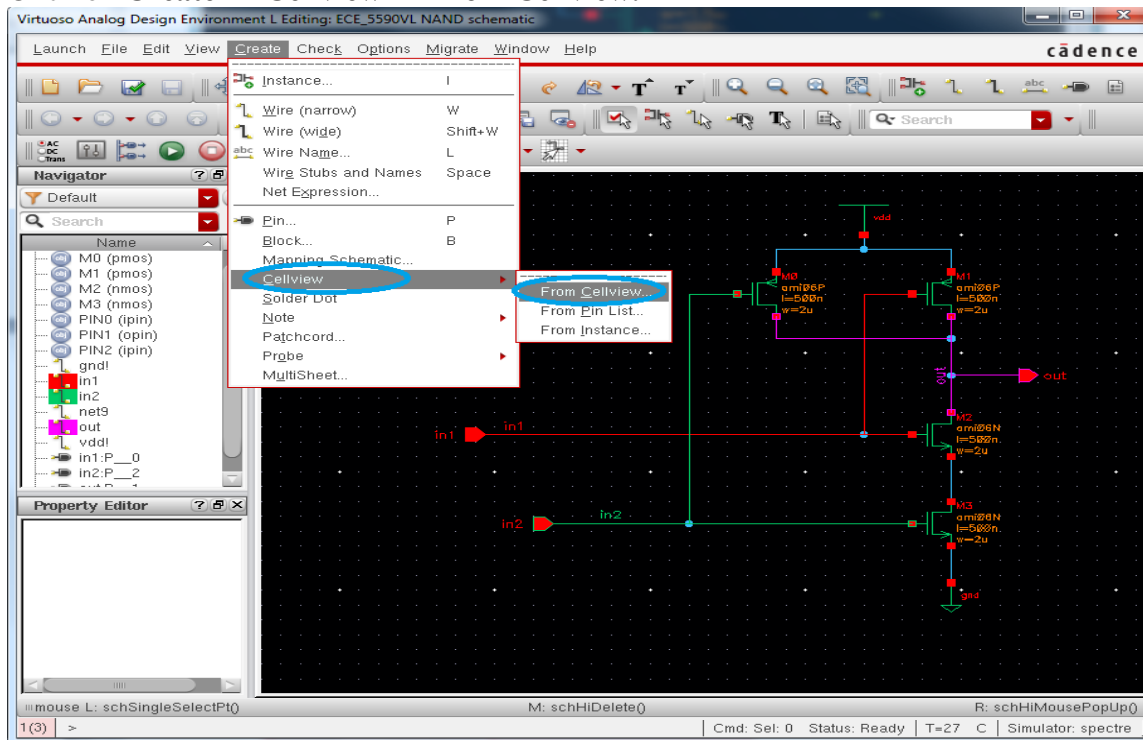
Click on **Create** → **Cellview** → **From Cellview**.



 On the **Cellview From Cellview** window type **NAND** for cell name and click **OK**.



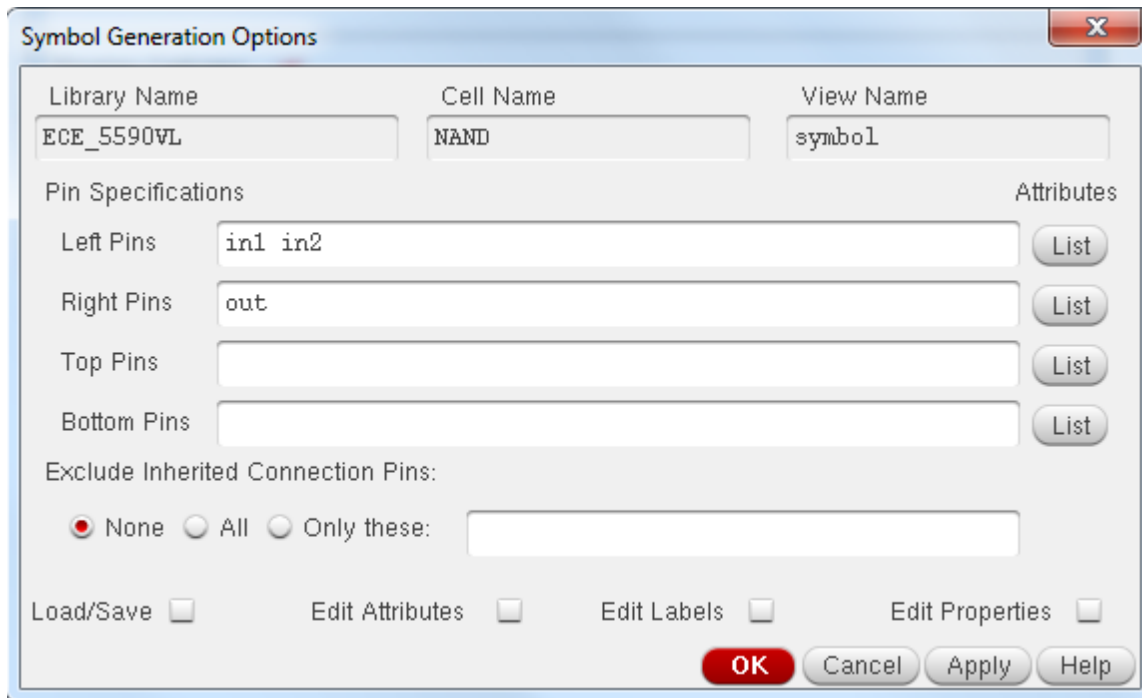When the **Symbol Generation Options** window appear, click **OK**.



The dialog box is titled "Symbol Generation Options" and has a close button (X) in the top right corner. It contains several input fields and checkboxes for configuring symbol generation.

Library Name: ECE_5590VL

Cell Name: NAND

View Name: symbol

Pin Specifications:

Pin Specification	Value	Attributes
Left Pins	in1 in2	List
Right Pins	out	List
Top Pins		List
Bottom Pins		List


Exclude Inherited Connection Pins:

☒ None ☐ All ☐ Only these:


Load/Save: ☐ **Edit Attributes:** ☐ **Edit Labels:** ☐ **Edit Properties:** ☐

Buttons: OK, Cancel, Apply, Help

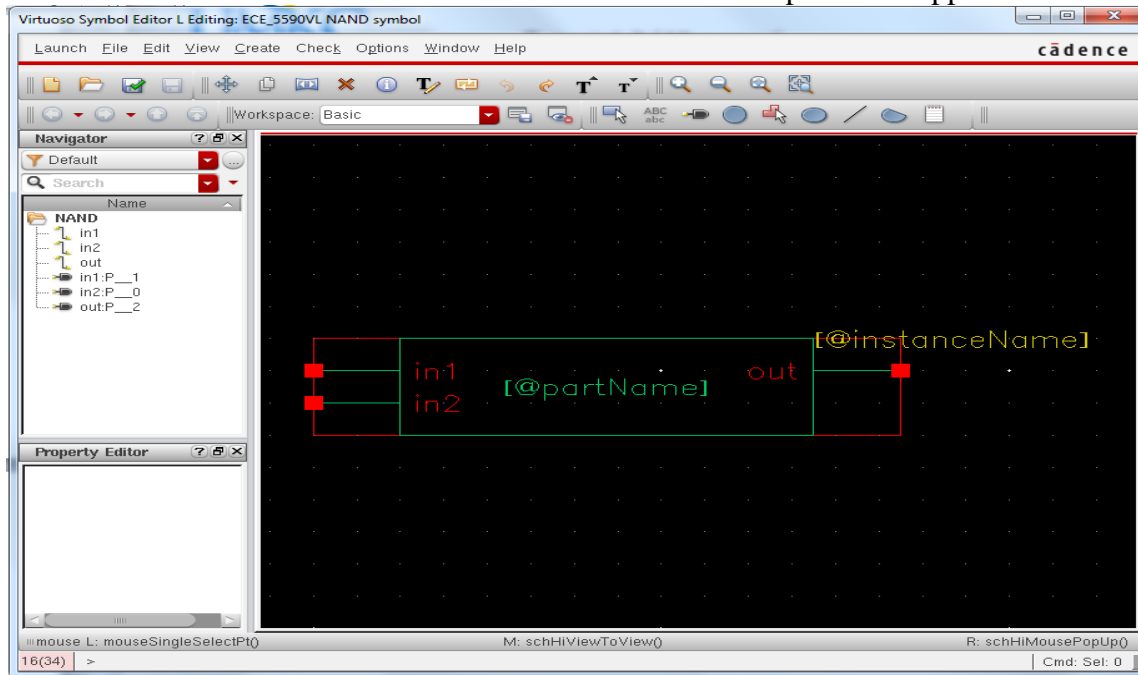
A new **Virtuoso Schematic Editor** window with default shape should appear as follow.



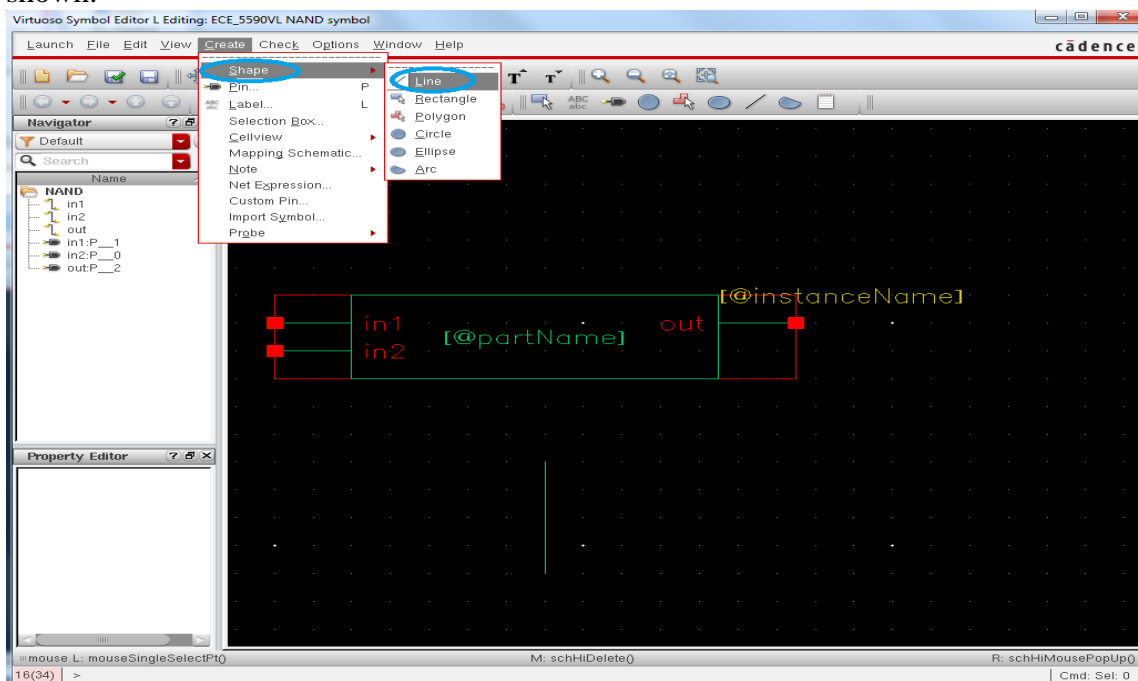
We can change the default shape in to the shape of a NAND that we are familiar with in the past. To do just that, click on **Create** → **Shape** → **Line**. Double click to place and draw the line as shown.



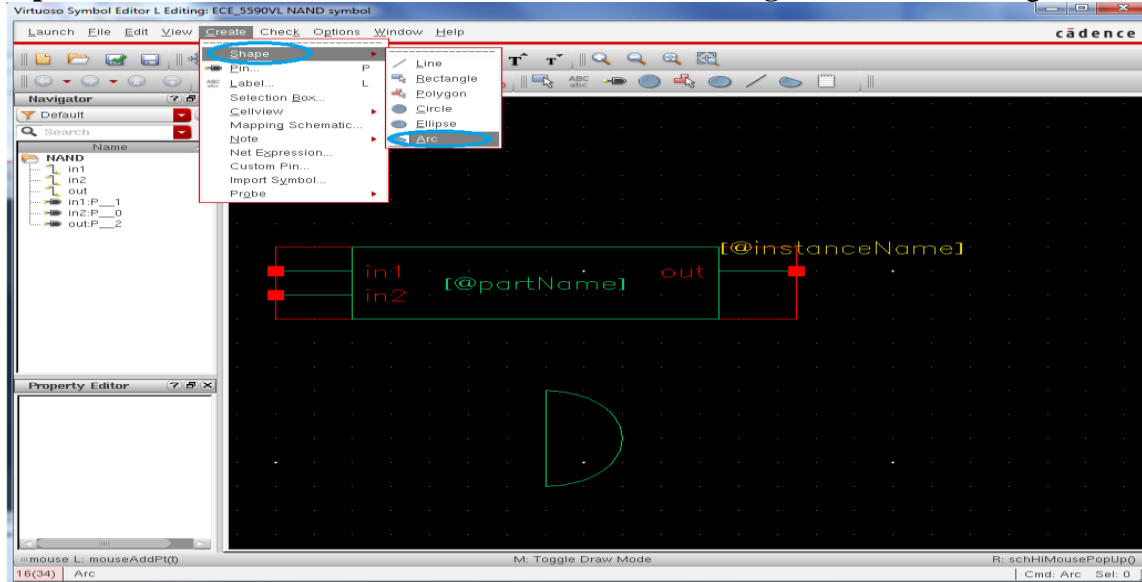
Then, click on **Create** → **Shape** → **Arc** and draw an arc as shown. To draw the **arc**, click the **top-end** of the line and the **bottom-end** of the line and **drag** the mouse to the right.



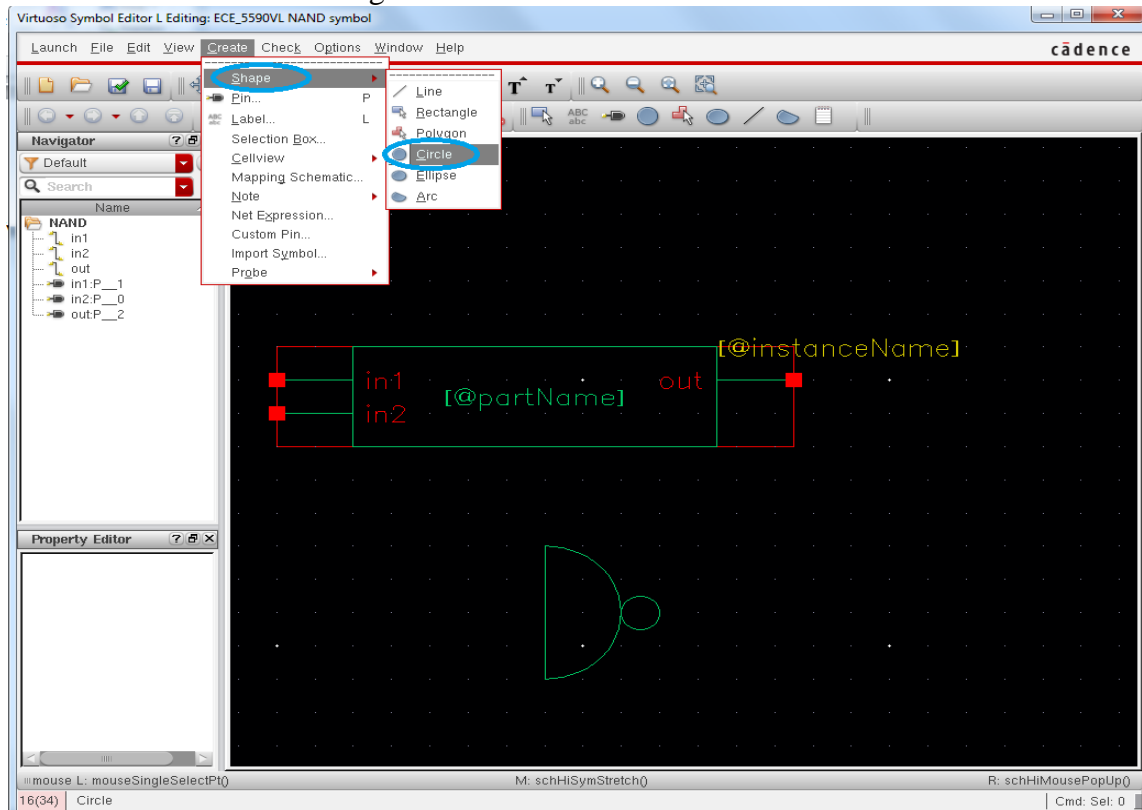After that, click on **Create** → **Shape** → **Circle** and draw circle as shown. Type **m** and click on the circle to move it to the right location



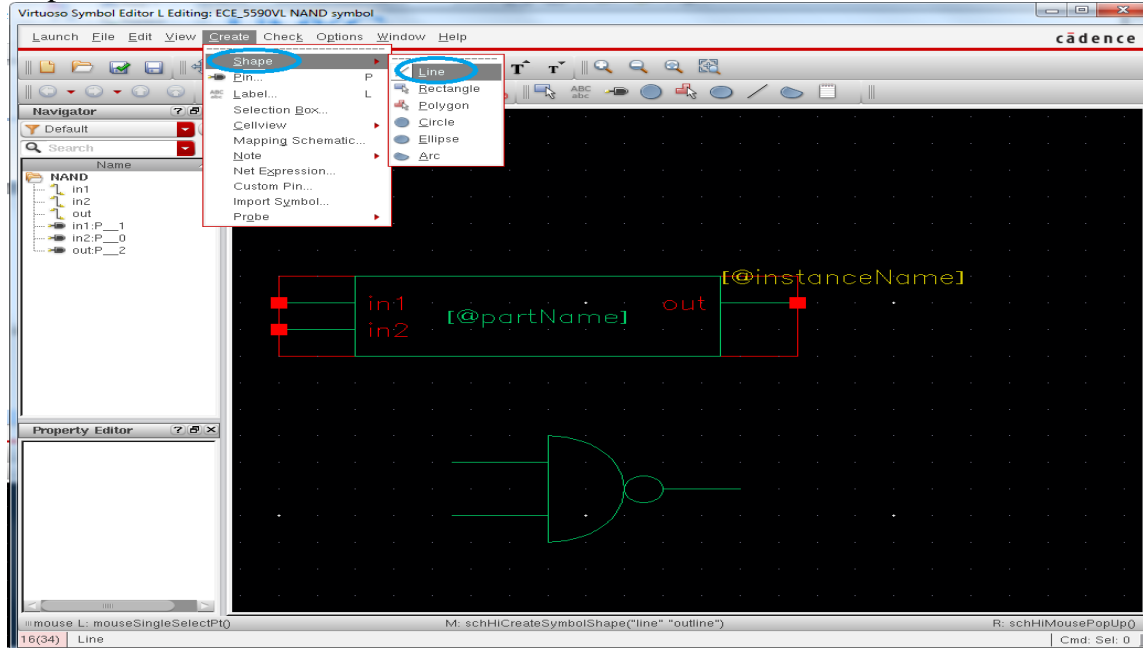
Click on **Create** → **Shape** → **Line**. Double click to place and draw the two input lines and the output as shown.




Now you can delete the default **red lines** and **green boxes** and move the **inputs** and **output** pins to the **new shape**. Also, try to rearrange the inputs and output pin names by dragging them using your mouse.

(Note: do not delete the **[@partName]**, **[@instanceName]** labels, and the **inputs** and **output** pins.)


So, your design should look as follow.

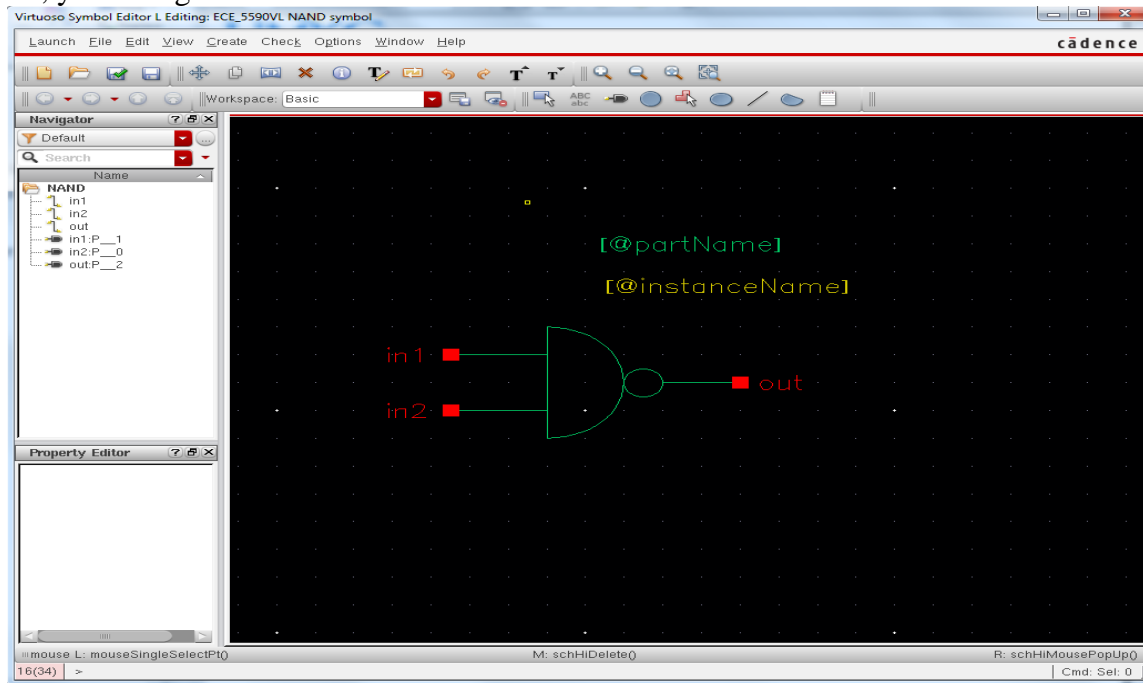

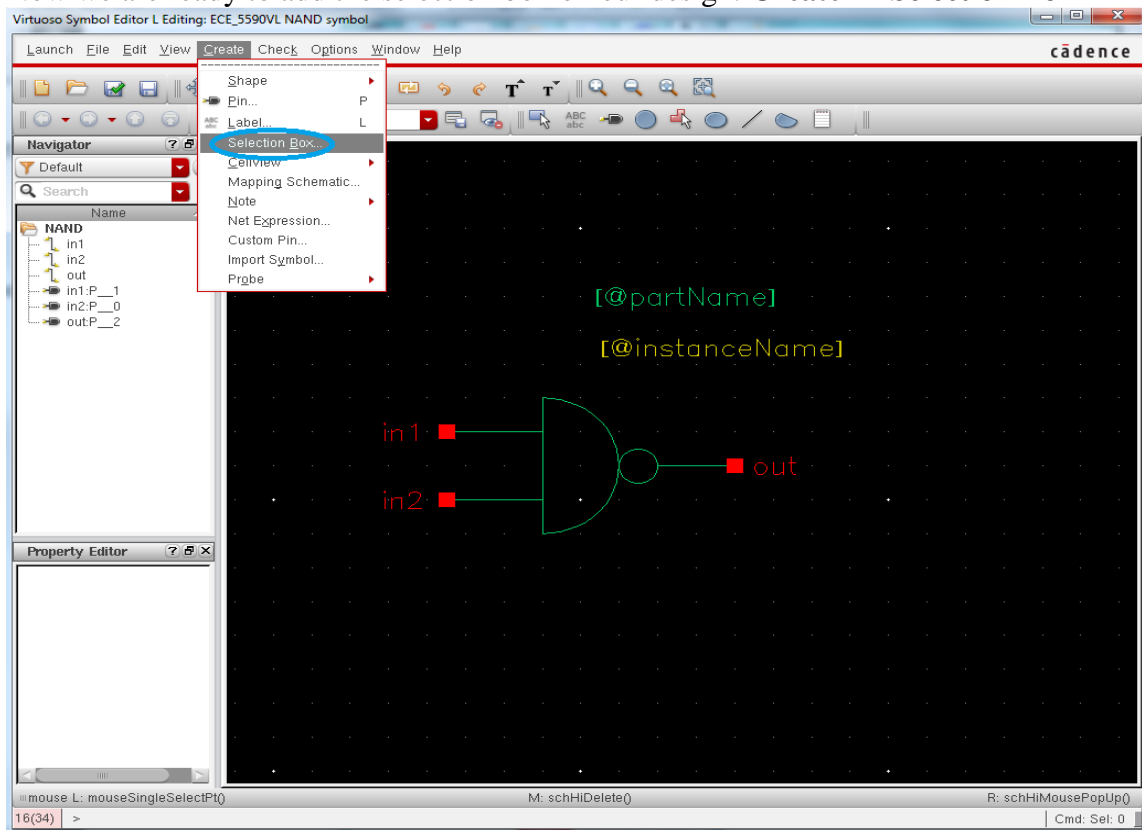
Now we are ready to add the selection box on our design. **Create → Selection Box**



Click on the Automatic

 


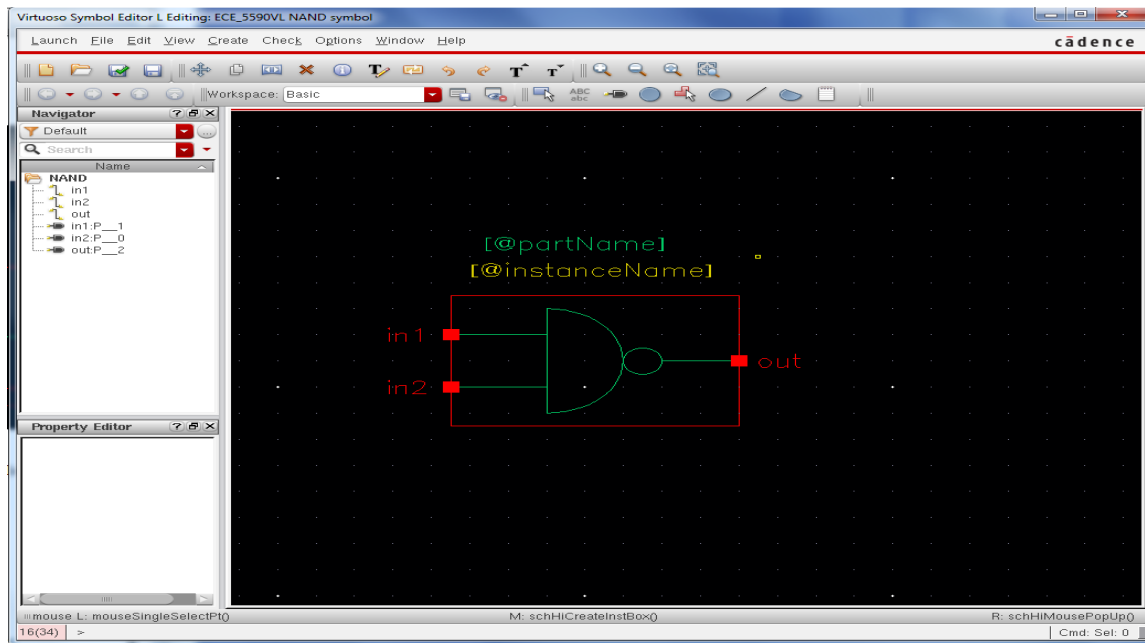Then, by dragging any of the four sides of the rectangle and adjust your design to match the symbol shown at the bottom. After that click on **Check and Save** button to see if your design is free of error.




Simulating the NAND symbol


Go to file

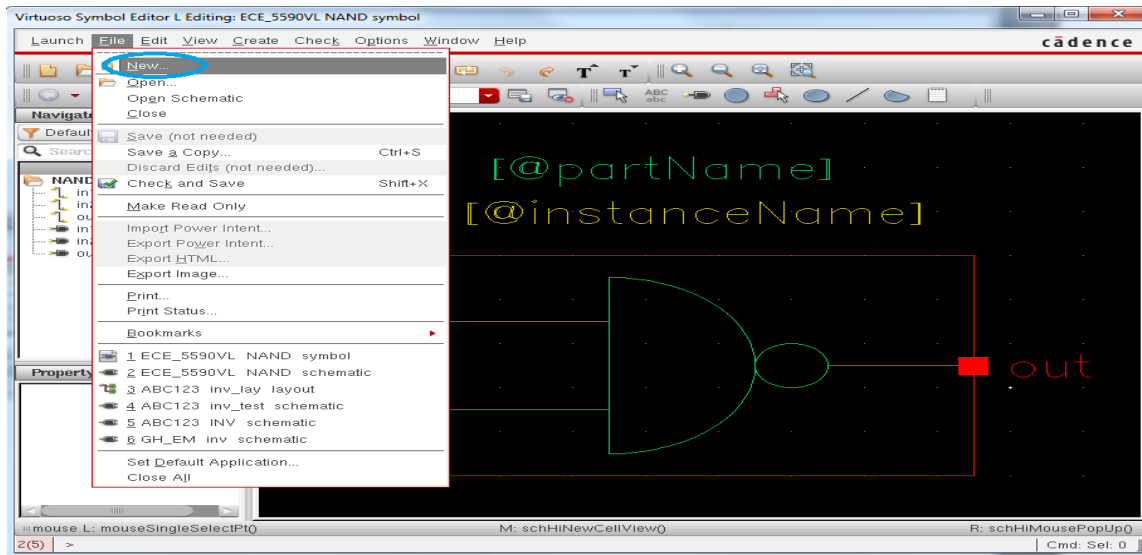

 
On the **New File** window select schematic from **Type** selection, and under **Cell** name wire **NAND_test** then click **OK**




Create → Instance → Browse → Hide

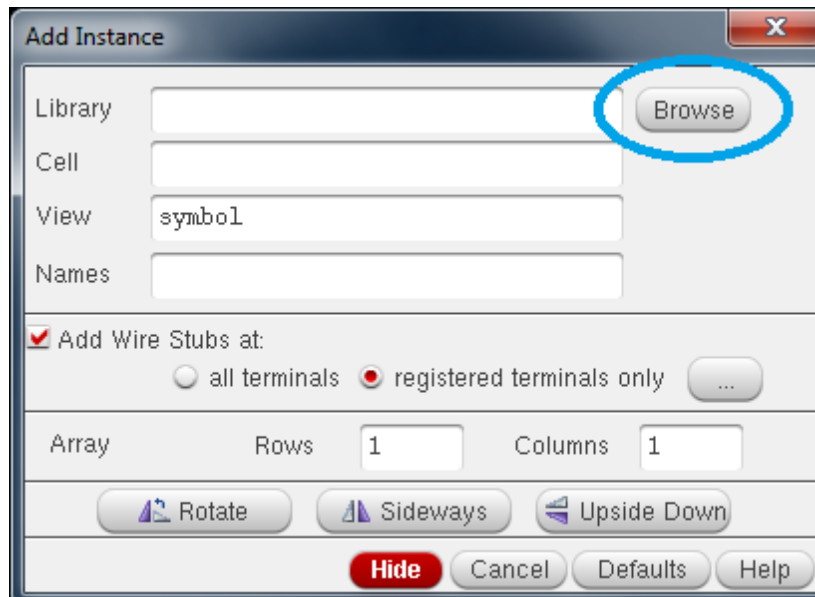

 
On the **Component Browser** window under the **Library** options, select **ECE_5590VL** (or whichever your library name). Then, click on the **NAND** symbol. After placing the symbol tap on **Esc** key on your keyboard to exit out of the command.



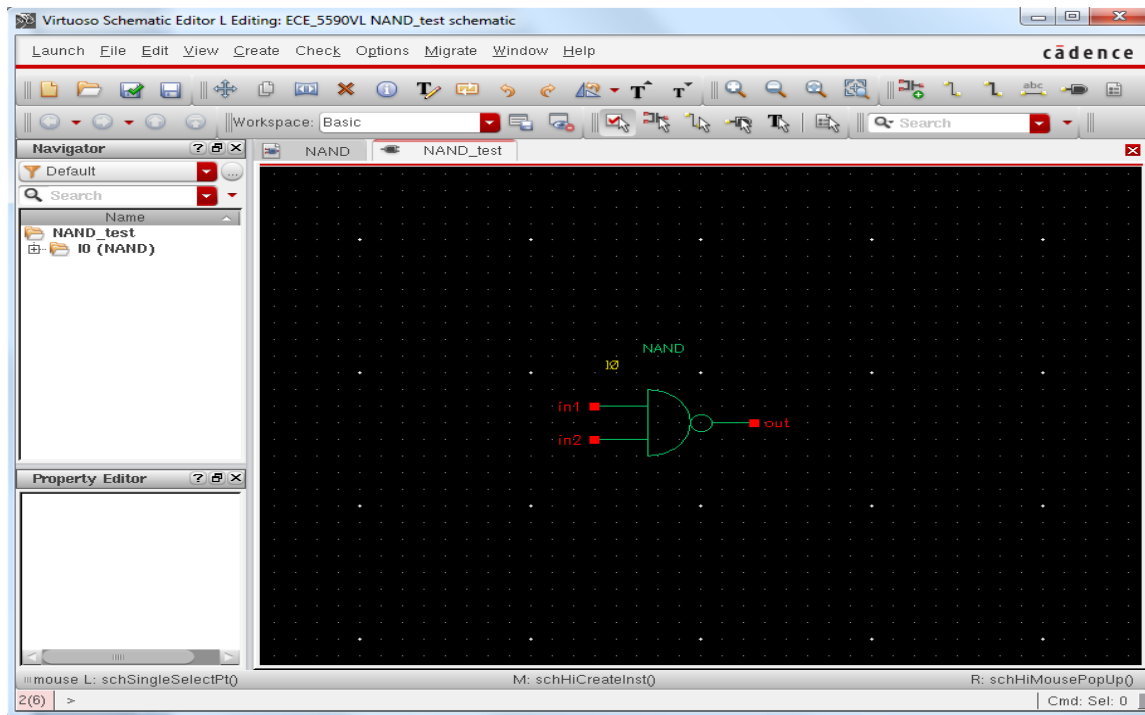
The **Virtuoso Schematic Editor** window should look as follow.



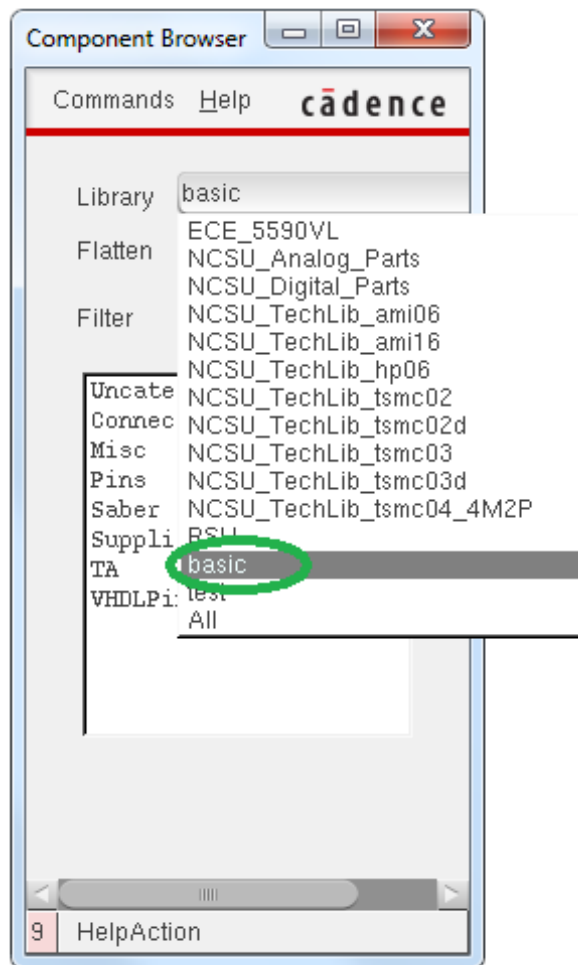
Now, we need to put back the **vdd**, **gnd**, **vdc** and both **vpulse** and enter the proper values that are given above. Also click on **Create** → **Instance** under the **Component Browser** select **basic**.




Then, click on **Misc** → **noConn**

 

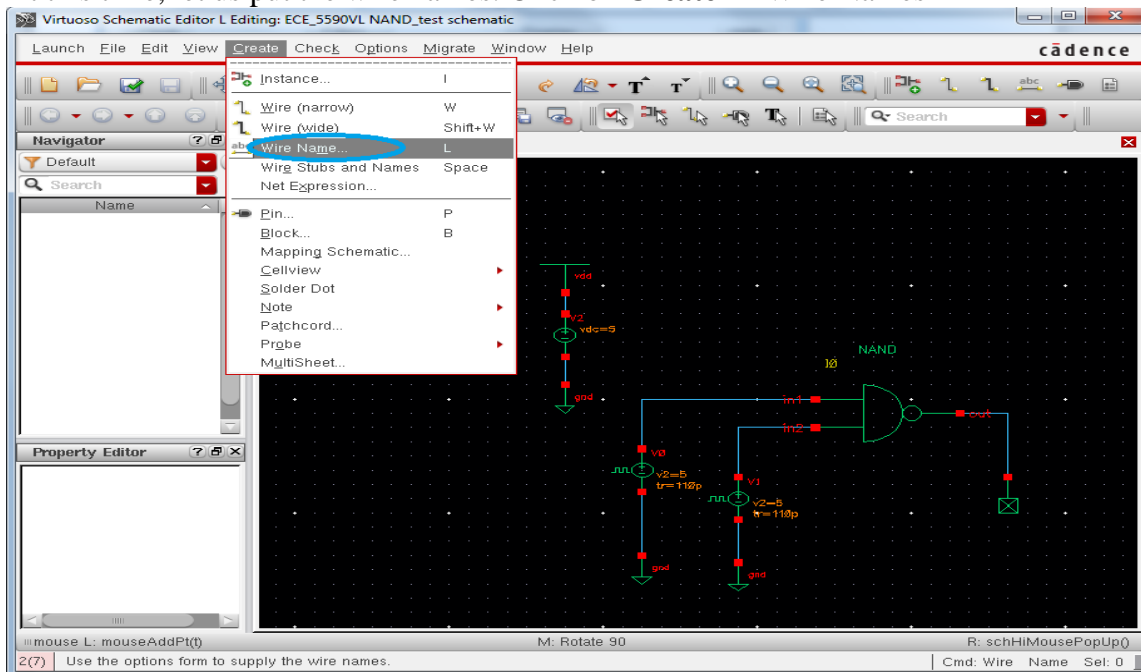
At this time, let us put the wire names. Click on **Create** → **Wire Names**



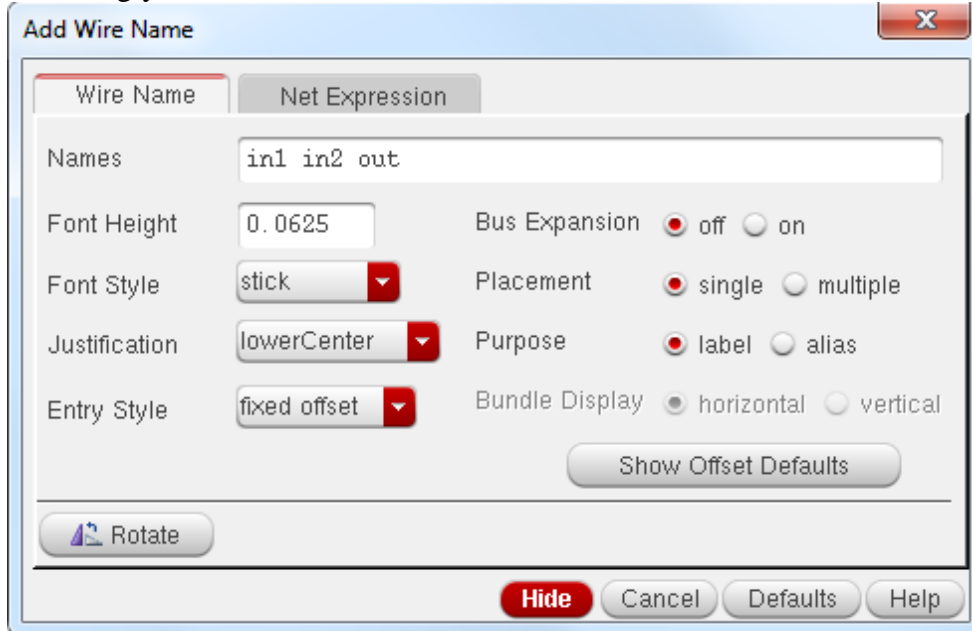
On the **Add Wire Name** window add **in1**, **in2** and **out** then click **Hide** and place them accordingly on the **Virtuoso Schematic Editor** window.



Now, your design should look as follow

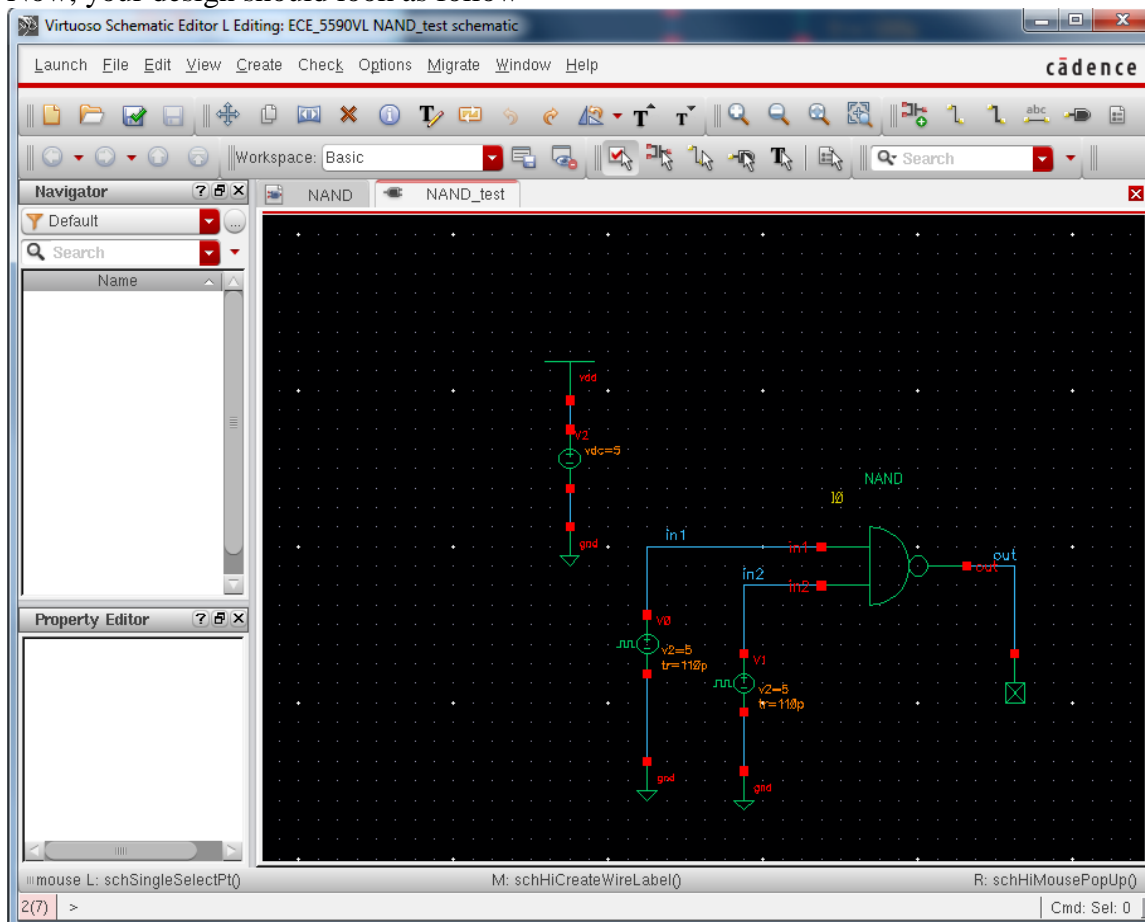

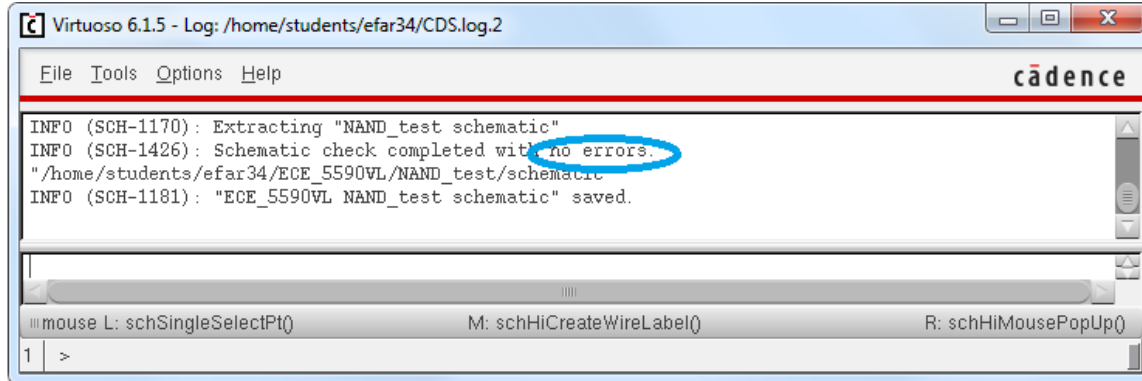Click on **Check and Save** button to conform if your design is free of error



Follow the simulation procedure given above and conform your result

You are done with the schematic part of the tutorial!

Acknowledgment:

This tutorial was prepared with the reference previously prepared by Dr. Daniel Leon-Salas and Mohammad Benyhesan.

